
 


Bits on speed!

...0010010101...

 

SERDES design in advanced CMOS technologies


SERDES design in advanced CMOS



- Motivation & Challenges
- Architectural solutions
- Implementation details
- Future trends & remarks

Internet traffic

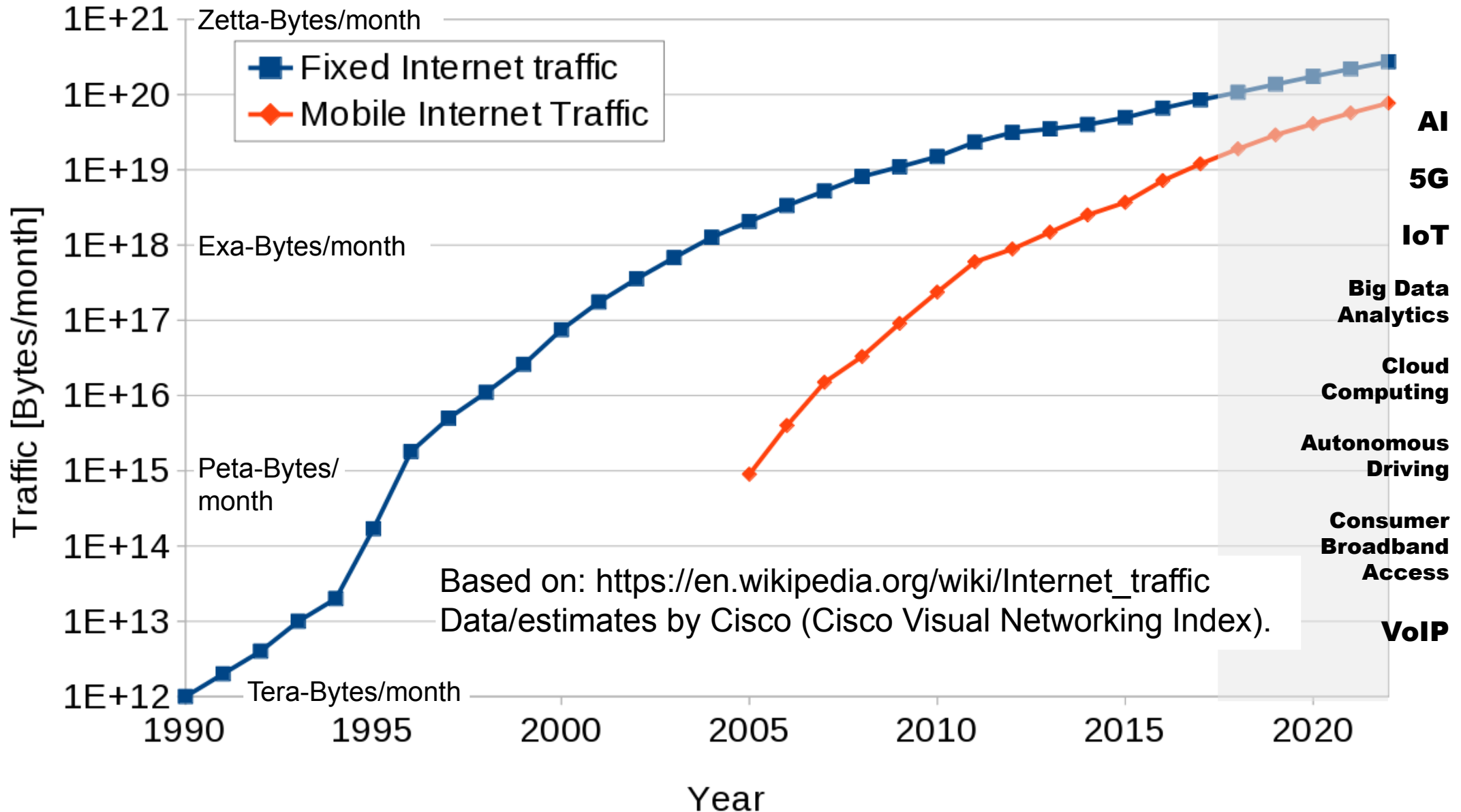
IP Traffic 1990-2022 (predicted: 2018-2022)




Interconnection speed – buses and networks




Computer Buses

 


Storage

 

Peripherals

 


Local Area Network

 

High Speed Interconnects today

 
- 99.99% of data processing to-date is silicon transistors
- 90% of long distance signaling is optical
- Networks use different media to overcome their limitations
 - Chip-to-chip, intra-board, backplane, “short” cable interconnects still electrical
 - Move to optical for “longer” distances
- “Longer” becomes shorter at every generation
 - Tighter integration within the package
 - Integrated optics (silicon photonics)



Picture: OIF CEI-56G Application Note


CHIP-TO-CHIP COMMUNICATION SPEED
HAS BECOME THE MAJOR BOTTLENECK
IN IMPROVING OVERALL PERFORMANCE !

Hierarchical network organization

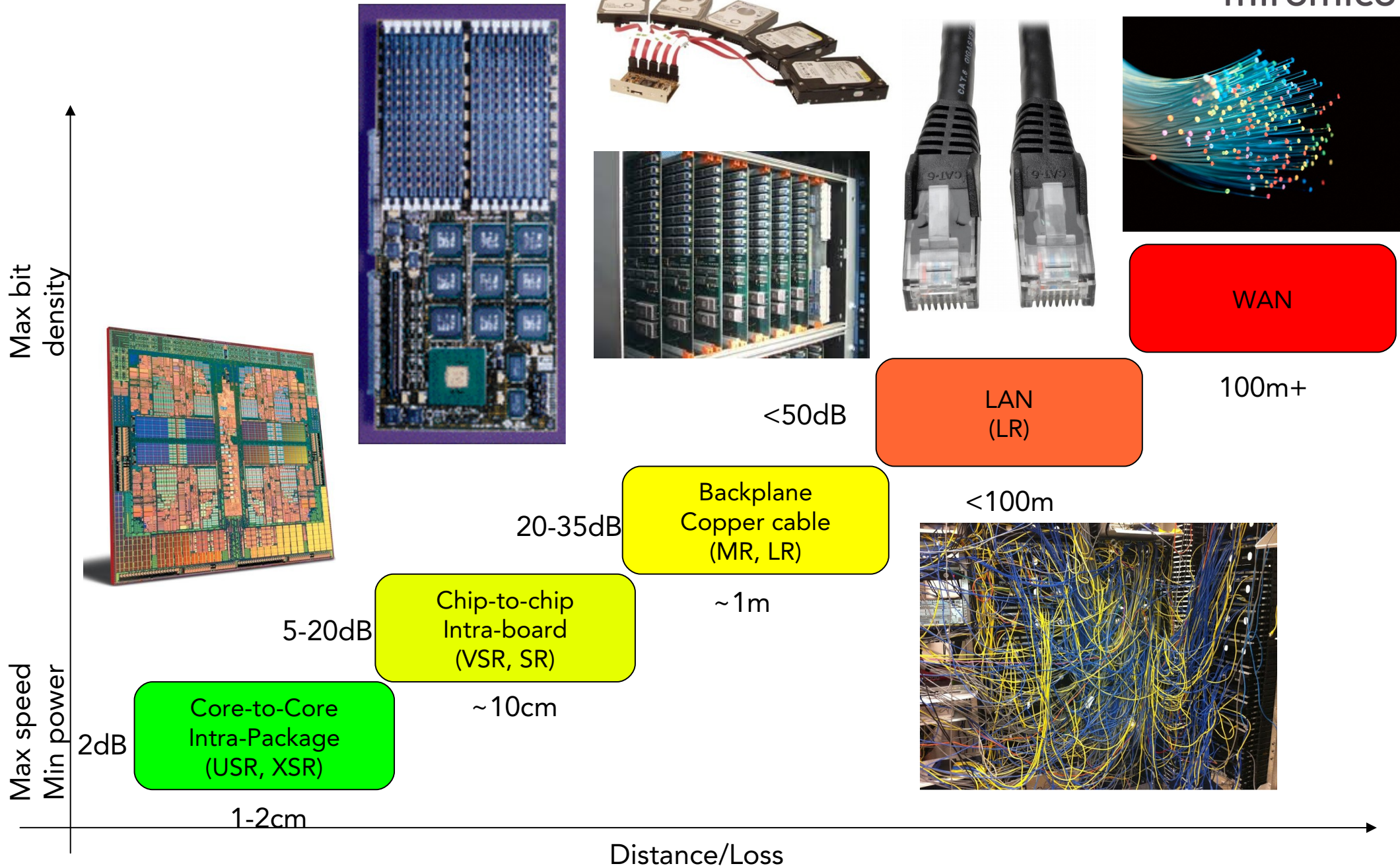

Challenge for the I/O Designers

- *Need to double data-rate every 2-3 years, while satisfying other constraints*
- Same total system cost:
 - Increase complexity in silicon before going to fancy new materials!
- Same total power:
 - Limited by package type, cooling system, etc.
 - ...but also by norms & regulations (cannot be too loud!)
 - Power limit capped at ~125W / chip (which is easily reached by a 150-way network-switch in 14nm CMOS, 50% from the I/Os!)
- Same chip size:
 - Doubling data-rate roughly doubles the number of associated gates, but also greatly increases the complexity of required equalization, FEC schemes, etc.
 - A 150-way network-switch in 14nm CMOS is roughly 25mm X 25mm bare die, 30% from the I/Os (cannot be much bigger than that!)
- Same package size:
 - Higher frequency typically means higher problems related to interference, cross-talk, signal integrity and calls for bigger packages
 - A 150-way network-switch in 14nm CMOS has a 62.5mm body-size package (cannot be much bigger than that!)
- Lower Signal-to-Noise Ratio:
 - Higher bandwidth, higher device noise
 - Higher loss in the channel

 


SERDES design in advanced CMOS




- Motivation & Challenges
- Architectural solutions
- Implementation details
- Future trends & remarks

The generic Serial-Link

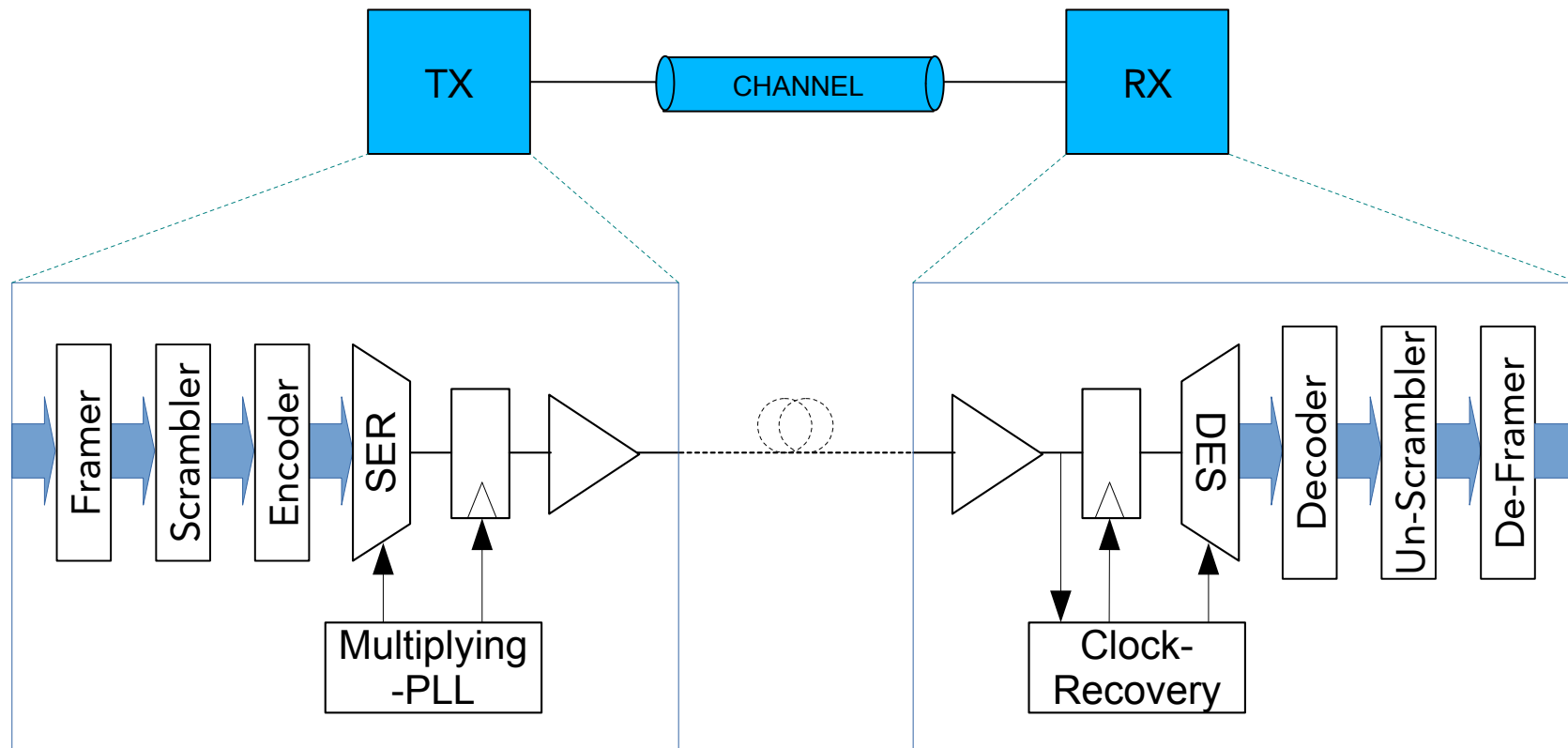


- Why “serial” links? Embed the clock into the data to avoid time skew limit!
 - In “parallel” links the clock is sent separately (eg. source sync., system sync., etc.)
 - However timing-skew limits the speed (<Gbps range) and/or distance (USR, XSR)
 - No time-skew in serial links! BW \gg Gbps (but: need encoding and clock-recovery)
 - Serial links have been systematically replacing parallel ones in the past few decades
 - What counts is the datarate-per-pin (...the communication is massively parallel anyway!)

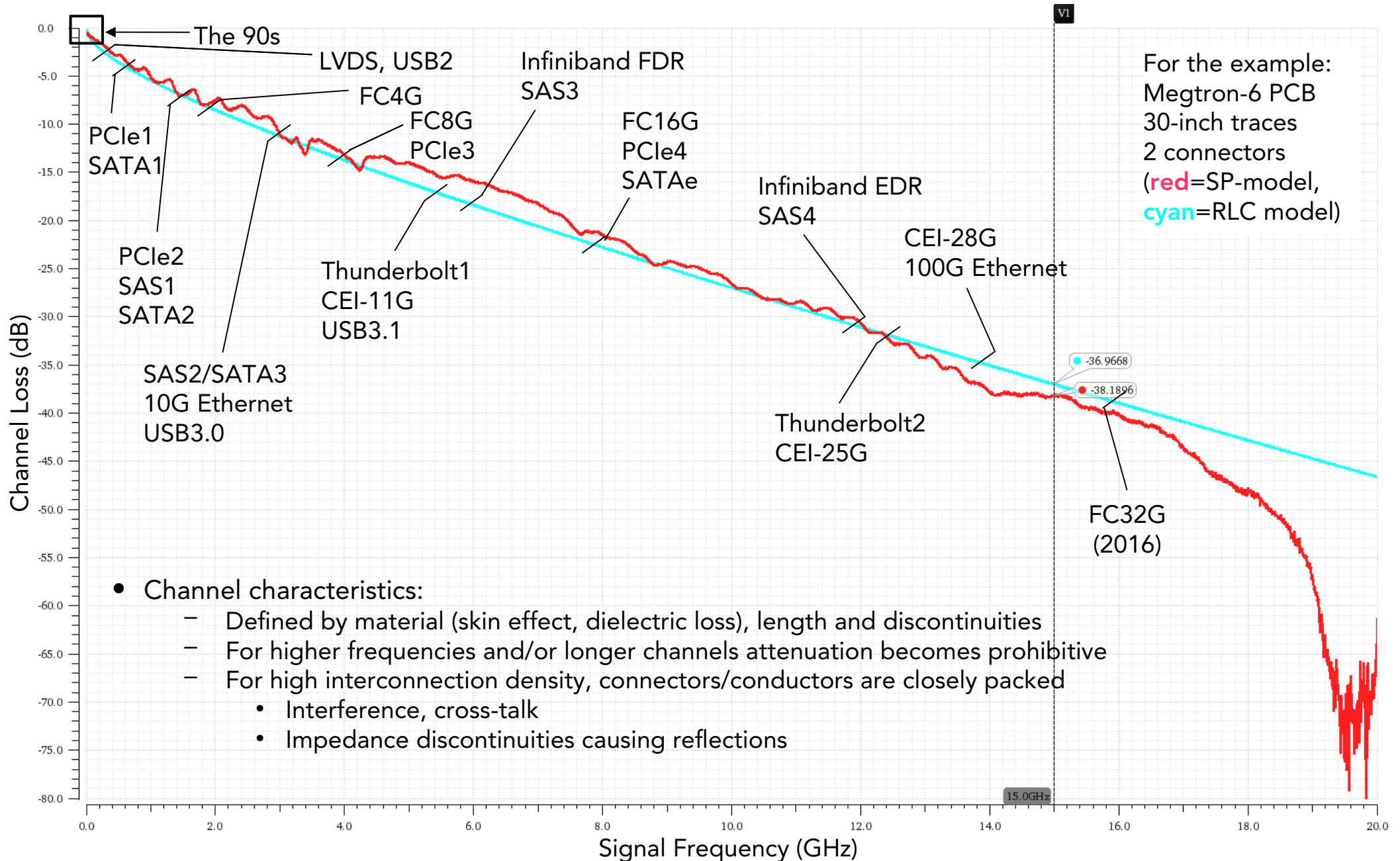Typical Electrical Interconnect characteristics




Effect of channel loss on the signal?


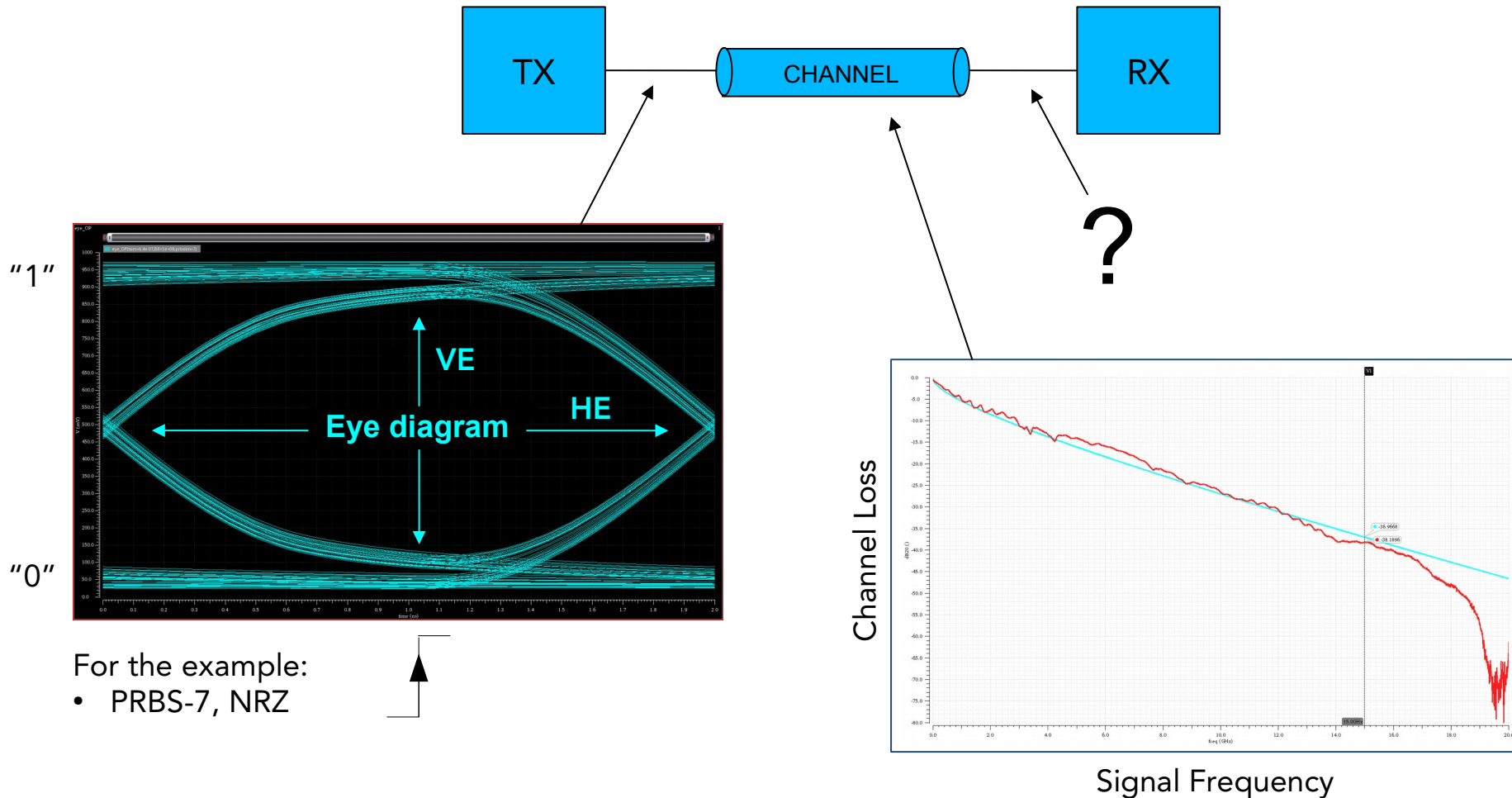


- RX input signal must have sufficient Vertical- and Horizontal-Eye openings:
 - VE must accommodate for slicer sensitivity, offset and noise
 - HE must accommodate for clocking accuracy and signal jitter



Effect of channel loss on the signal?

 




Inter Symbol Interference (ISI)

  

Inter Symbol Interference (ISI)

  


Equalization of the channel (example)

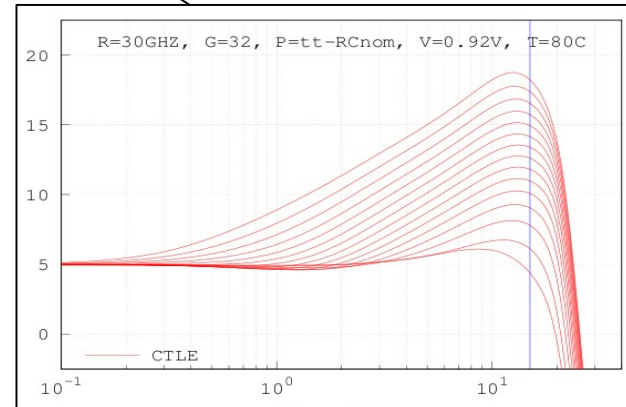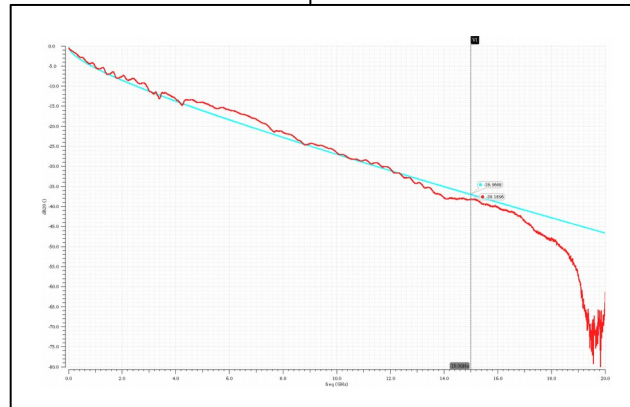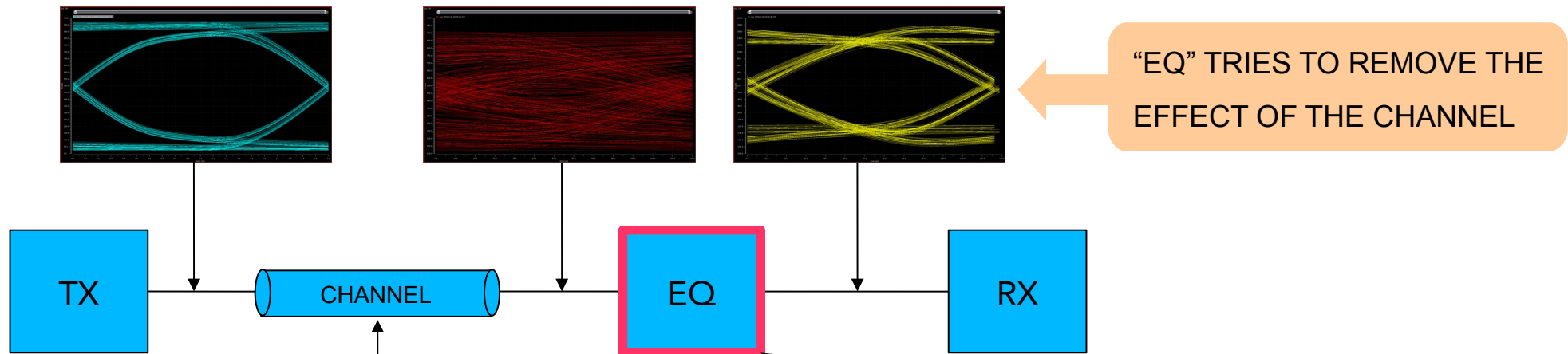

EX.: BY APPROXIMATING THE INVERSE CHANNEL RESPONSE (Linear Equalizer)

Equalizer Classification

 

Different kinds:


- Linear vs. Non-linear
- Continuous time vs. Discrete time
- Transmitter vs. Receiver equalization
- Synchronous vs. Asynchronous
- Feed-Forward vs. Feedback-Loop
- Manual vs. Adaptive
- Passive vs. Active
- ...

Most popular acronyms:

- **FFE** → Feed-Forward EQ
- **CTLE** → Continuous-Time Linear EQ
- **LTE** → Long-Tail EQ
- **DFE** → Decision-Feedback EQ


Feed Forward Equalization (FFE)

- It's a **Finite Impulse Response (FIR)** filter:
 - ISI is linear (can be corrected by filtering)
 - Boost bits coming after a transition (HF "pre-emphasis" or LF "de-emphasis")
- Most often seen as de-emphasis **TX-FFE**:
 - Easier to implement in TX (digital domain)
 - Helps for receiver linearity
 - But: Degrades EMI/crosstalk
 - Difficult to be made adaptive
 - Nevertheless widely used whenever the channels response is sufficiently well known in advance (mostly the case)

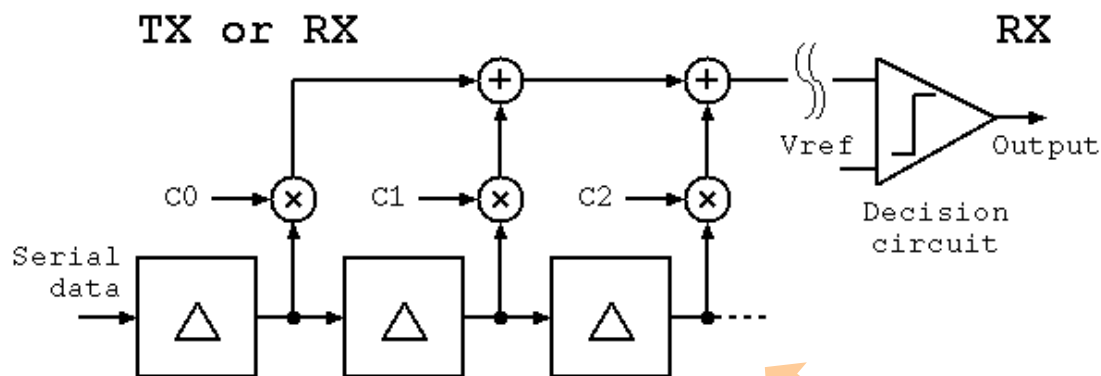


Normally limited to 3-4 taps



WITHOUT FFE

 


WITH FFE

 


Feed Forward Equalization (FFE)

  

Adding FFE at 8Gbps

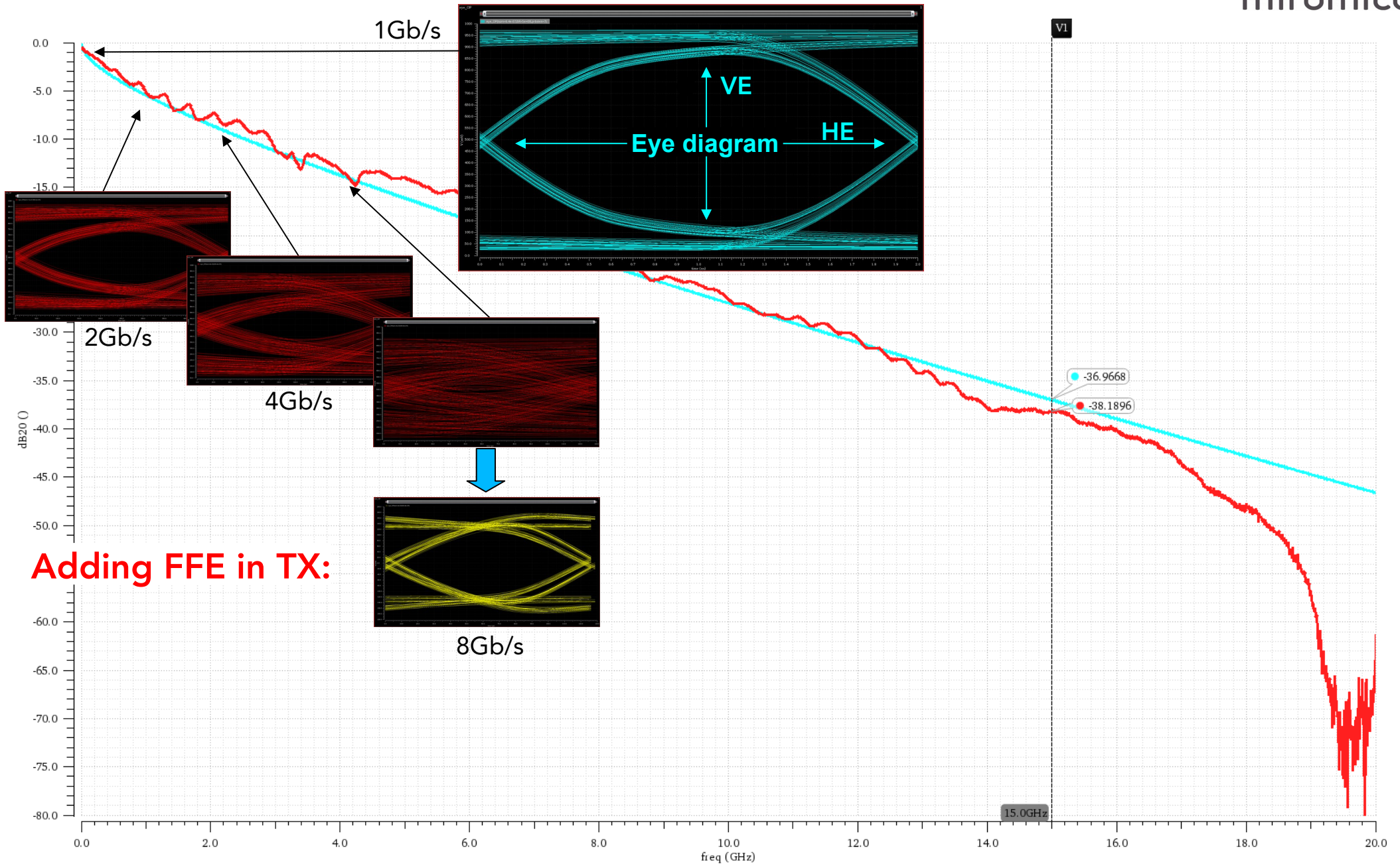

Doubling the rate (16Gbps)

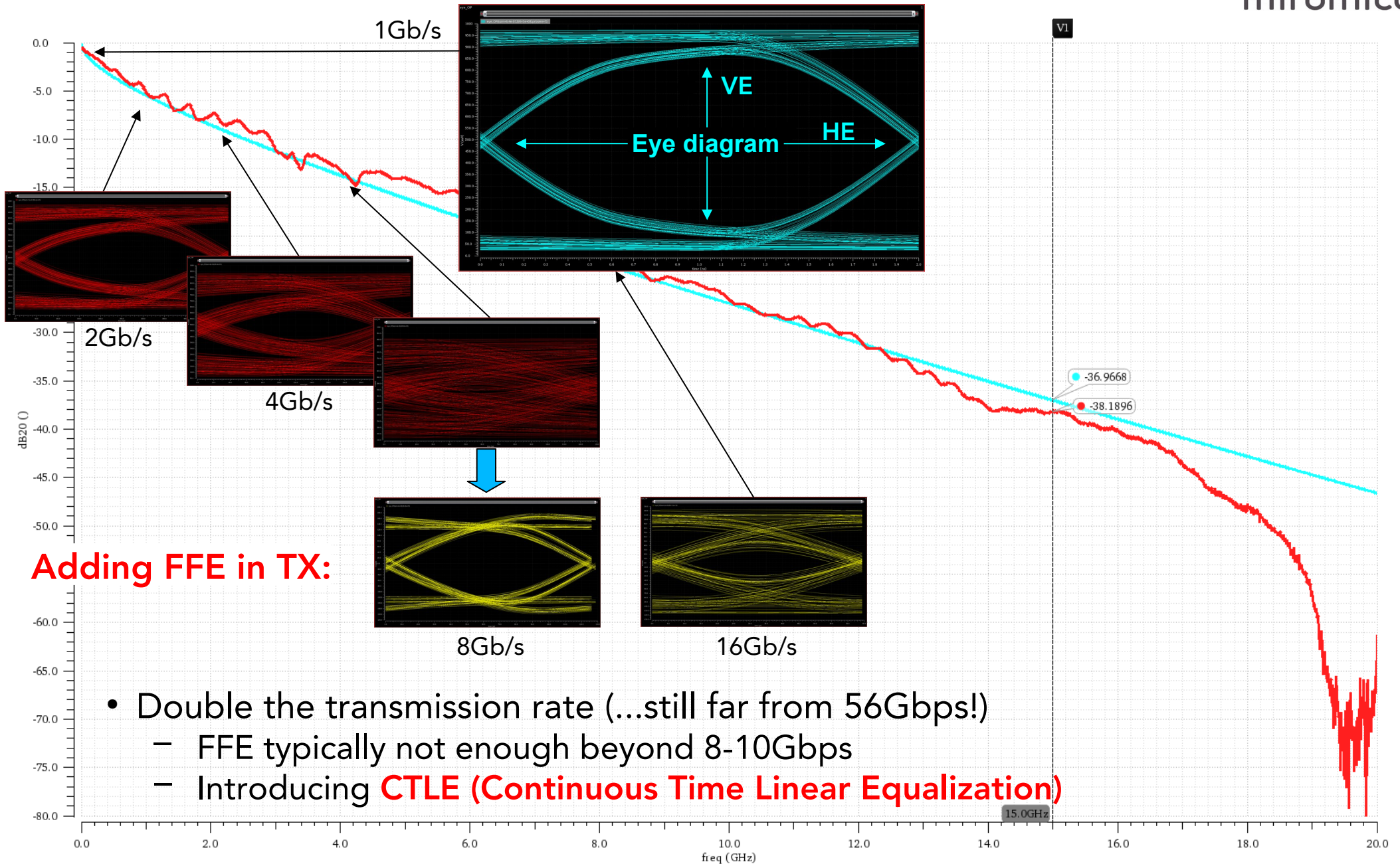


Adding FFE in TX:



- Double the transmission rate (...still far from 56Gbps!)
 - FFE typically not enough beyond 8-10Gbps
 - Introducing **CTLE (Continuous Time Linear Equalization)**

Continuous-Time Linear Equalization (CTLE)

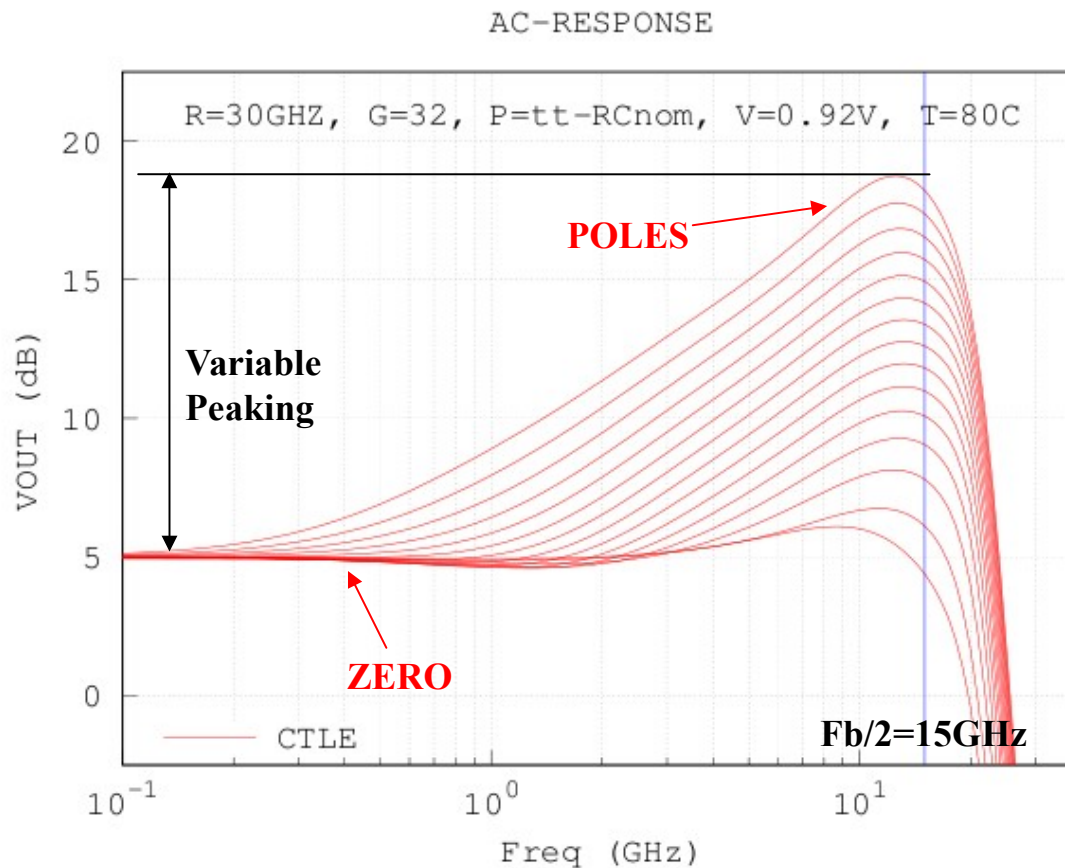- CTLE counteracts ISI by **boosting high-frequencies** around $F_{\text{baud}}/2$
 - Contains at least one zero (peaking amp.), but can have more (LTE, ...)
 - Programmable transfer function, for adaptation
 - Unfortunately amplifies noise/interference at the same time
 - Channel equalization typically requires up to 10-12dB peaking (min. across PVT)





  Continuous-Time Linear Equalization (CTLE)





Long-Tail Equalization (LTE)

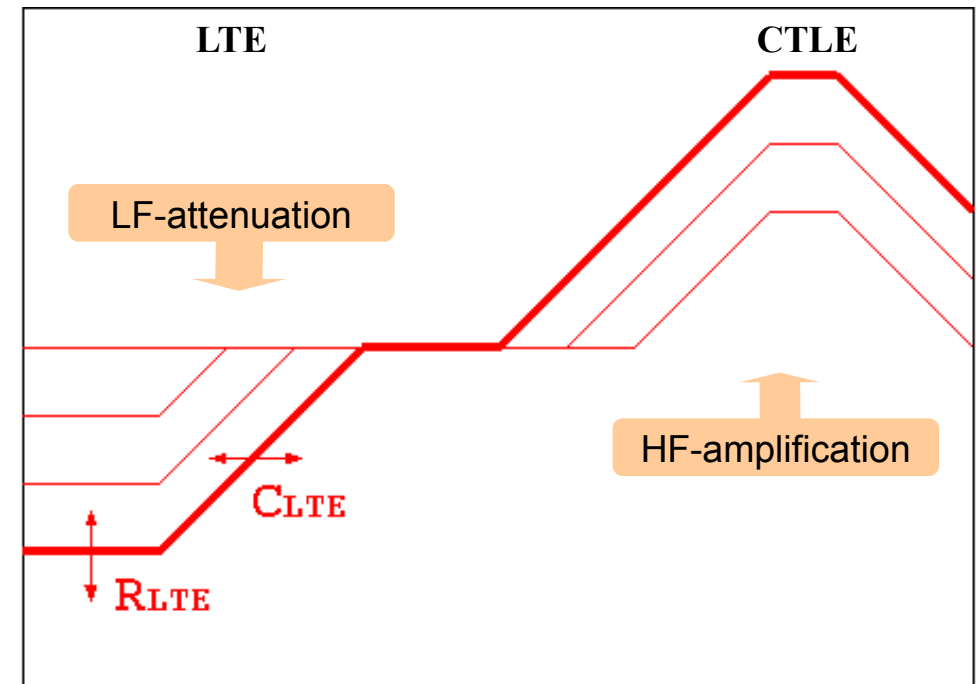 - LTE is also a Continuous-Time Linear Equalizer
 - Naming underlines that it operates **outside the reach** of other equalizers
 - Most manufacturers add LTE function at 16~20Gbps node (and beyond)
 - Addresses (roughly) low-freq channel attenuation due to skin-effect
 - Need up to 7-10dB emphasis in the mid-band & pole programmability (0.4~2GHz)




- Increases EQ capability of the CTLE by combining LF-dump & HF-boost
- Often requires bulky passive devices (RLC). Tends to become a luxury in modern technologies optimized for digital


Long-Tail Equalization (LTE)

  

Adding CTLE/LTE at 16Gbps

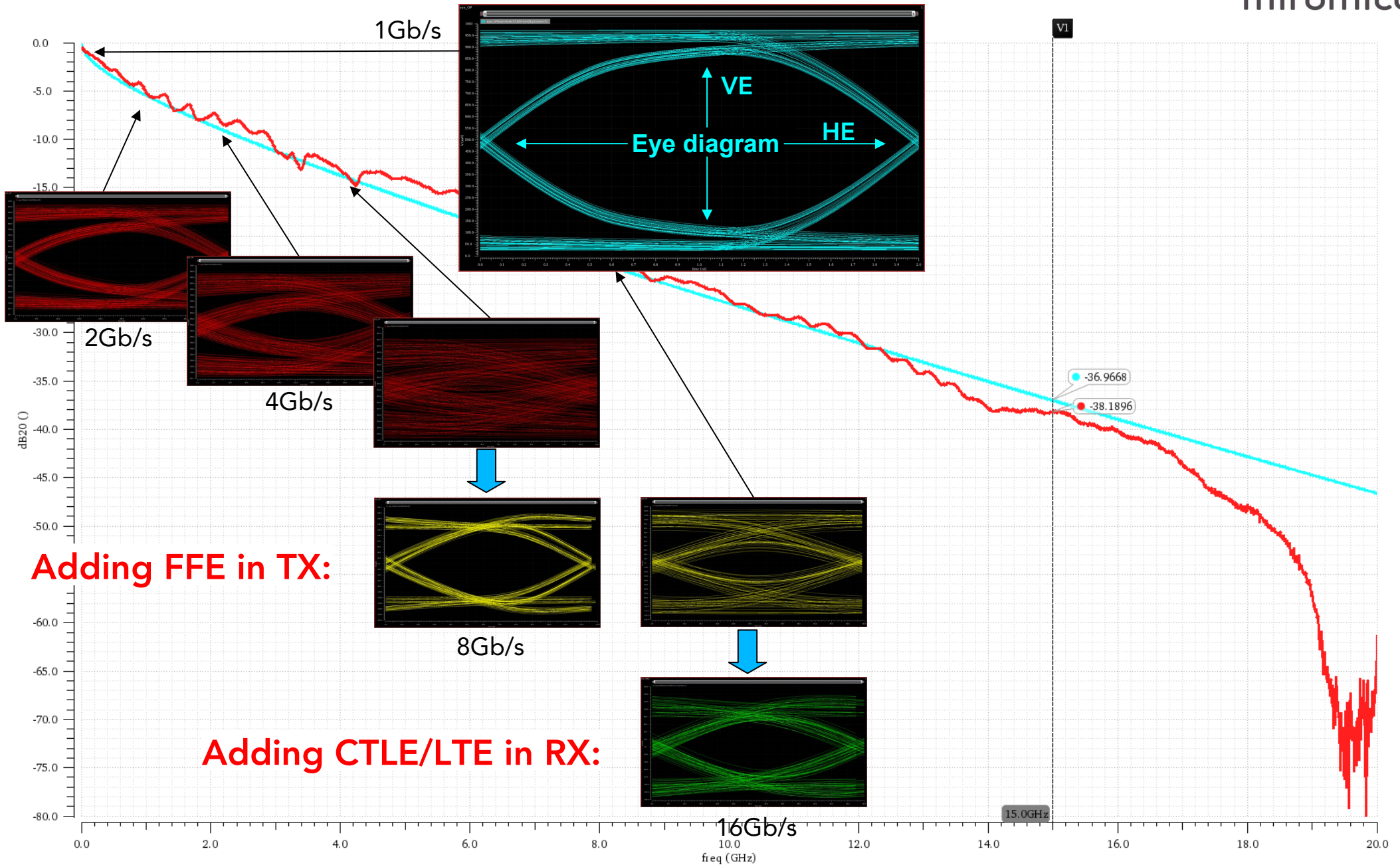


Doubling the rate (32Gbps)

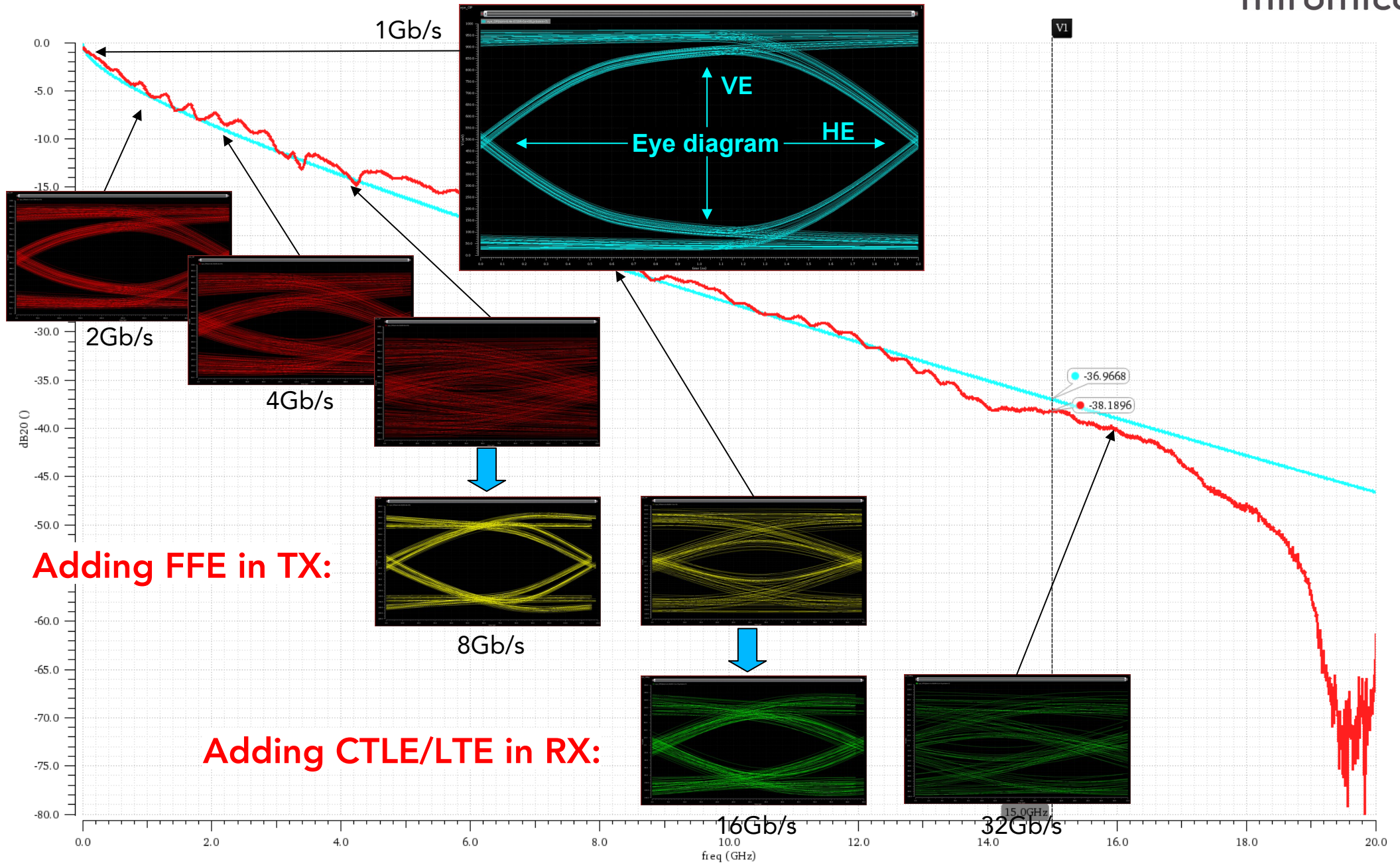


Decision Feedback Equalization (DFE)

- FFE/CTLE have several shortcomings:
 - On 35+dB loss channels simple FFE/CTLE equalization becomes very challenging
 - Amplify signal, noise and interference, without necessarily recovering SNR
 - It is anyway just a rough approximation of the inverse channel-response
 - CTLE/LTE tend to be bulky
- On the other hand: we really only need to **cancel ISI at the sampling point!**
 - If we “know” the previous symbols (the already received ones)
 - And we know how a single bit is distorted going through the channel (ISI)
 - We can calculate the ISI (using a FIR) and remove it from the incoming bit

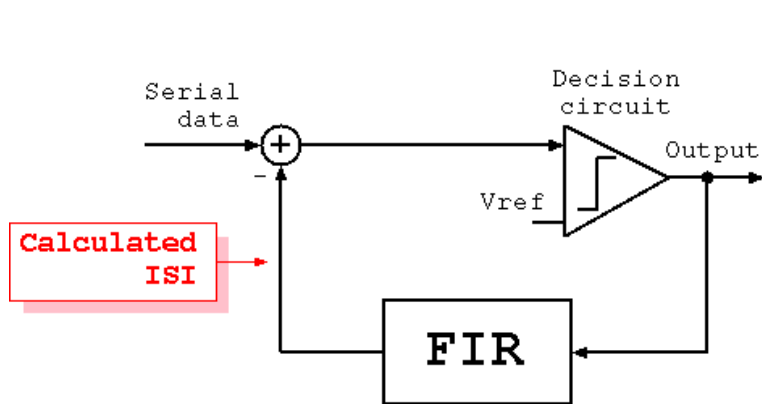


[Austin 1967]

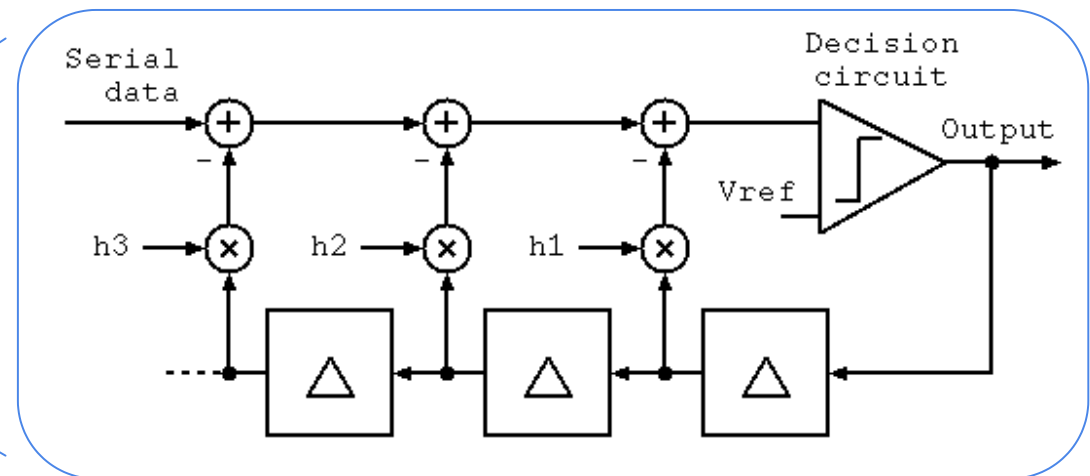


Delay → Scale → Subtract

Decision Feedback Equalization (DFE)

- DFE does not attempt to invert channel, just remove ISI before taking the decision
 - Does not amplify noise and interference
 - Can cope with an arbitrary channel response (takes care of reflections)
 - Time "depth" is limited by number of feedback taps (trade-off vs power)
 - Error accumulation problem (bursts of errors)
 - Time critical & power hungry (but feasible: demonstrated in CMOS down to UI~30ps)

 


Adding DFE at 32Gbps

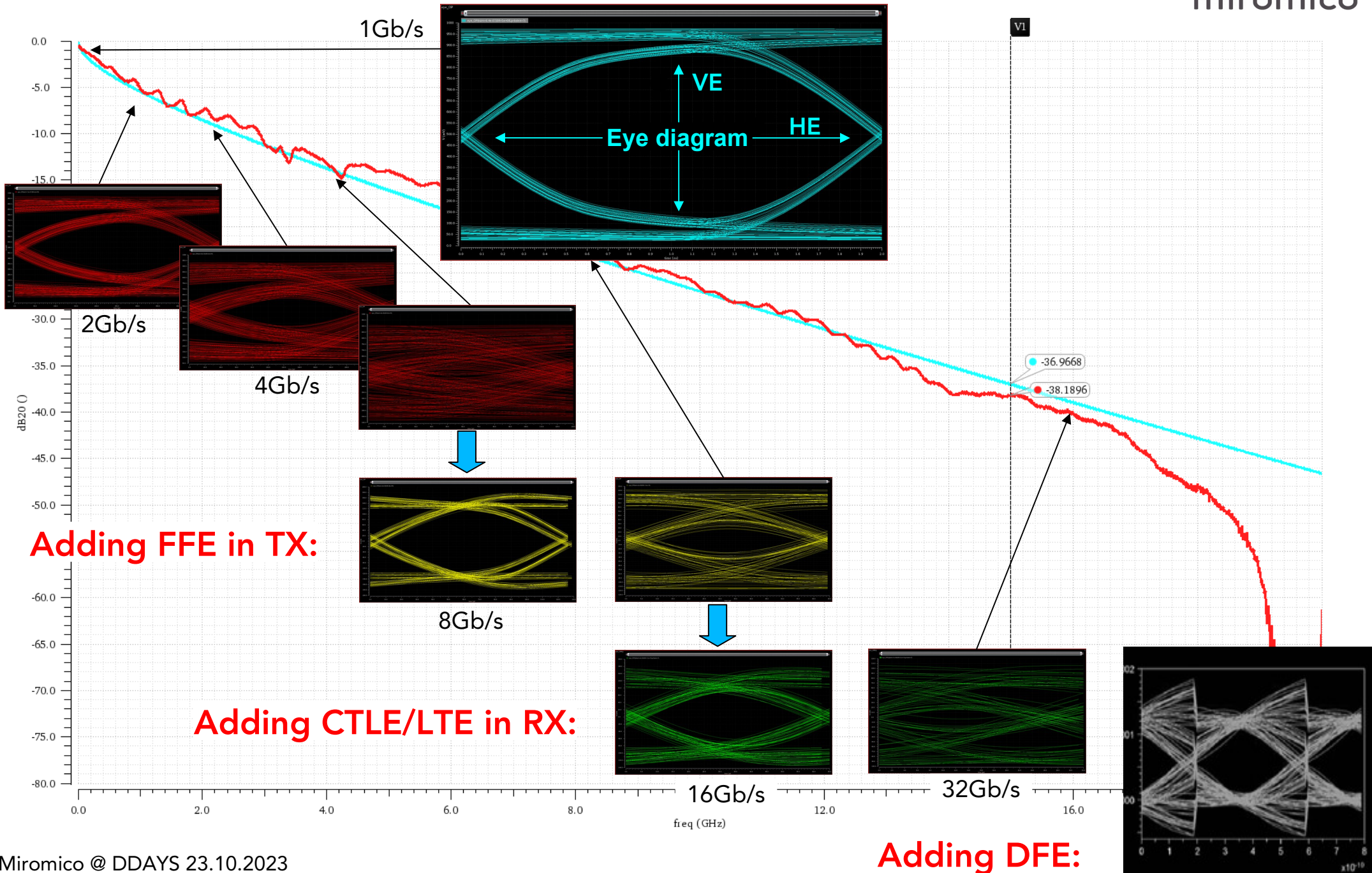

The right mix

	Advantages	Disadvantages
FFE	- Simple	- Non-adaptive - EMI, Xtalk
CTLE / LTE	- Adaptive	- Amplifies noise - Rough correction - Bulky
DFE	- No noise/xtalk amplification - Works on arbitrary channel	- Error accumulation - Complex, timing critical - Time-span limited by power

 - FFE/CTLE/LTE usually “just” functional to robust lock of CDR/DFE
- DFE has also limited applicability and tends to be power hungry
- **Combined use of different equalization types to obtain the best results**
- Other kinds of equalization exist but are not mentioned here




SERDES design in advanced CMOS



- Motivation & Challenges
- Architectural solutions
- **Implementation details**
- Future trends & remarks


Line Driver (DRV)

 




- Line termination
- ESD/LU protection
- Broadband adaptation
- CML vs. SST

Line termination & protection

- Current mode driver (CML)

 


- Voltage mode driver (SST)

   

- Line termination (& back-termination) is a MUST for high-speed wireline comm.
 - Less signal but integrity: broadband transfer, avoid multiple reflections
 - Parallel (CML) vs. Series (SST) termination
- Unfortunately ESD/LU protection is also a must for manufacturability
 - Protection diodes represent a significant parasitic capacitance
 - T-coils for better bandwidth & return loss [Galal JSSC 2004]
 - Series termination (SST) offers superior ESD protection


Line Driver

- Current mode driver (CML)

 

- CML stands for Current Mode Logic
- Unipolar (can use the fastest transistor)
- Purely differential
- Need higher voltage & current for same launch amplitude
- Input drive not directly CMOS (somewhat tricky)
- Asymmetric output drive


- Voltage mode driver (SST)

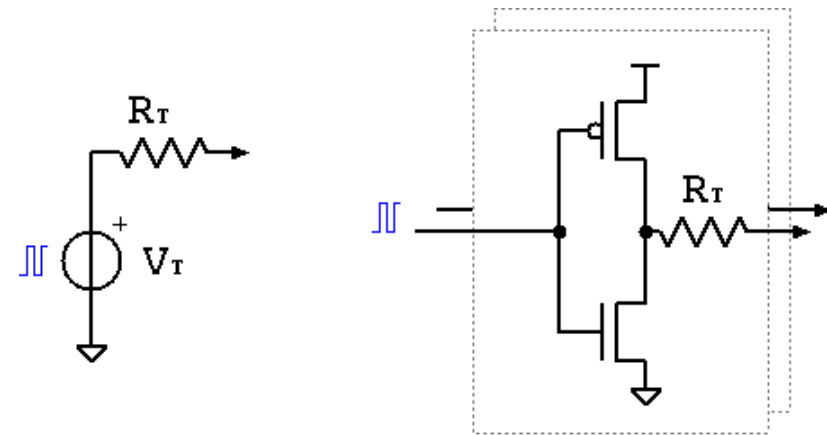

- SST stands for Series Source Terminated
- Switch output between supplies (need almost symmetrical devices). Uses the full supply
- Pseudo-differential
- Input drive is digital, CMOS compatible
- Symmetric output drive
- Switches impedance is part of the termination (more variable)


Line Driver

- Current mode driver (CML)

 

- Tail current sets the amplitude (can use segments to regulate amplitude while keeping constant current density)
- Impedance calibration done with prog. resistors (switches on top)

- Voltage mode driver (SST)

 


- Amplitude is defined by a ratio of unit elements (up's and down's) → intrinsic good matching. Function of the supply voltage
- Impedance calibration performed with programmable switches

ESD/LU protection


- CML

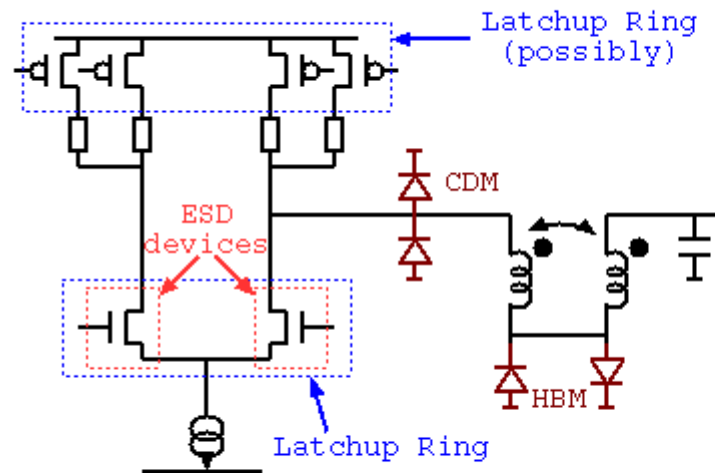- all driver diffusions are directly connected to the output PAD
 - only wire series resistance
 - current limiting is in the device
 - drain extensions
 - silicide mask
 - longer transistors
 - all diffusions are "HOT"
- Calibration switches have series R
 - LU ring needed depending on R




- SST

 - series resistors limit ESD discharge currents
- depending in the value of the R may still require LU rings




Feed Forward Equalizer (FFE)

 


Adding FFE to the Line Driver

- FFE
 - summation of $C_i b_i$ terms
 - envelope is well defined
- Use superposition:
 - split the driver in multiple slices
 - assign slices to coefficients
 - shift the bits from one to the next
- CML
 - easy to implement the summation
- SST
 - naturally segmented
 - the work happens in the digital domain
 - tricky to precalculate the configurations
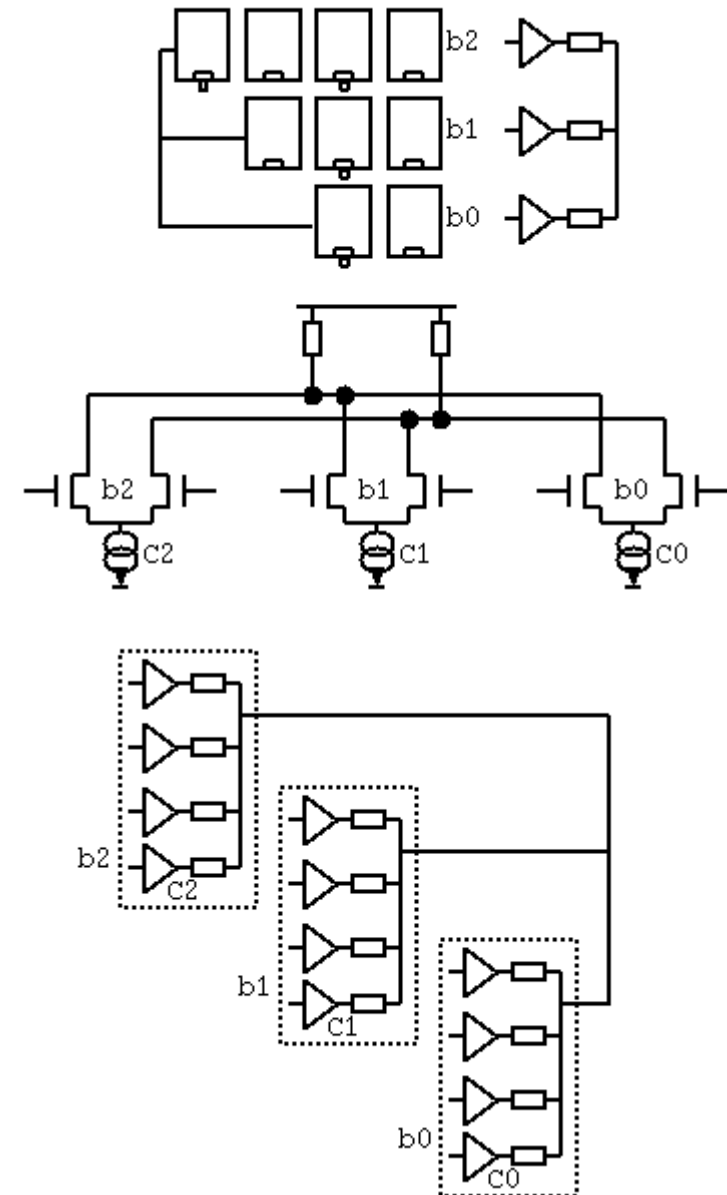
$$S = C_0 * b_0 + C_1 * b_1 + C_2 * b_2$$




RX → Analog Front End (AFE)

 

- Termination, ESD
- AC coupling
- AGC (attenuator, VGA)



RX → Analog Front End (AFE)

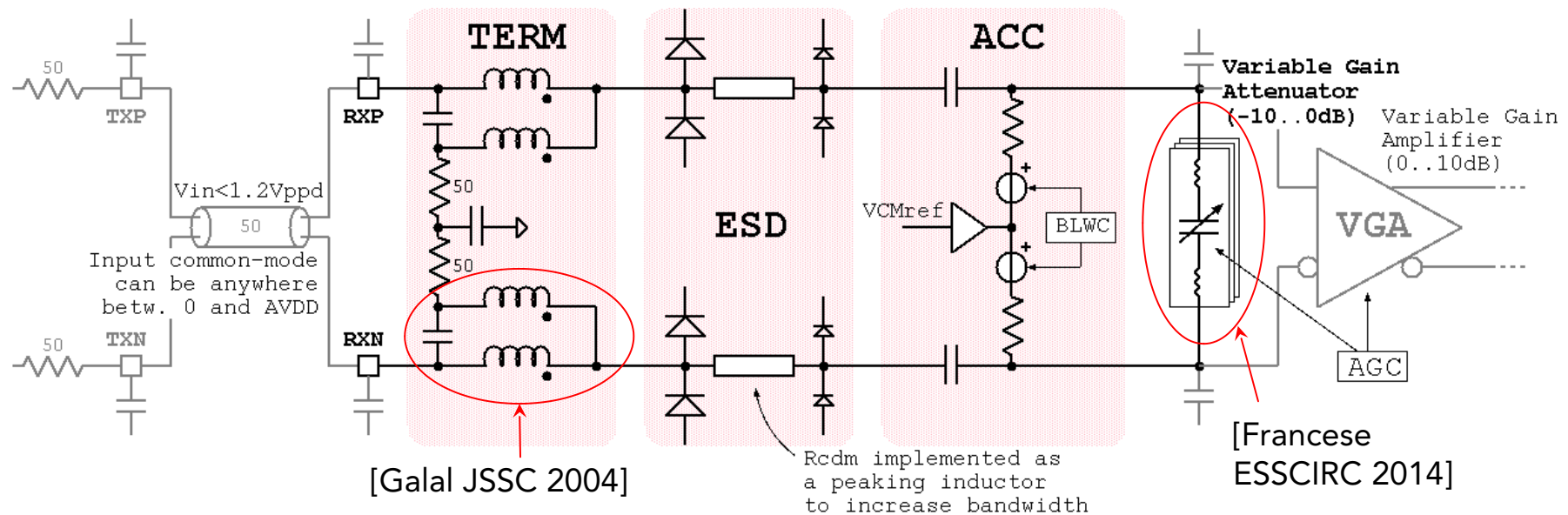

- Termination & ESD protection
 - Broad-band (from DC to baud-half and more)
 - Return Loss (common-mode & differential)
 - Two-stage ESD protection (HBM, CDM)
- On-chip AC coupling
 - AC-coupling: needed to decouple input common-mode of the VGA
 - On-chip: reduces system cost & area (can have >100 lanes / chip!)
 - On-chip: eliminates Z-discontinuity related to discrete cap on PCB
 - But: requires Baseline Wander Compensation (BLWC)
- Passive attenuation (supports AGC)
 - Capacitive divider (...careful not to destroy RL!)

RX → AFE → AC coupling (VCM & BLWC)

- Baseline Wander (BLW)
 - RC size limited by technology/area
 - Signal can be extremely broadband (plus: have to support legacy systems)
 - Spec: max(BLW) vs. transmission rate
 - Test: use OIF short-stress patterns
- BLW "compensation"
 - Can compensate BLW or avoid it altogether (IBM solution)
 - Level-shift signal directly from the pads (in a controlled loop)
 - Avoid discharge path by using floating voltage generators


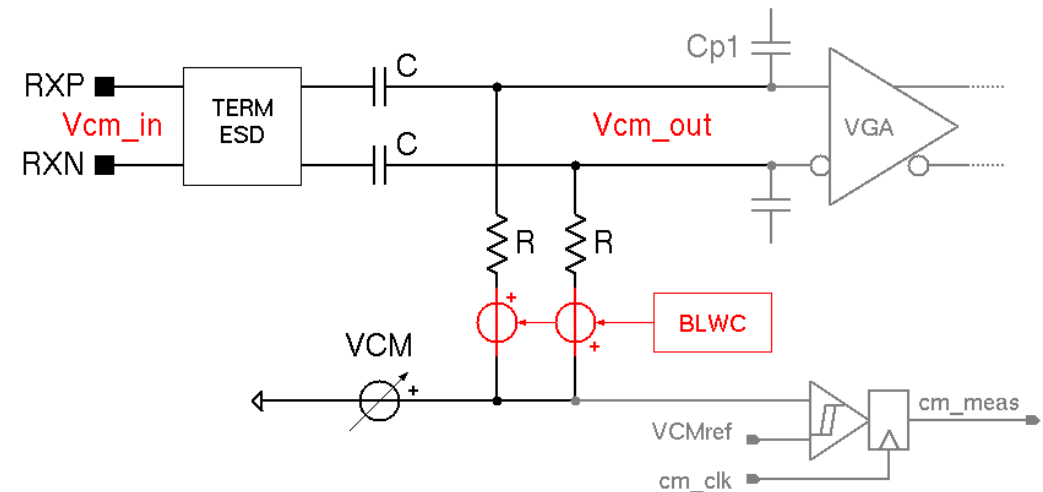
 


RX → AFE → AC coupling (VCM & BLWC)


- Baseline Wander (BLW)
 - RC size limited by technology/area
 - Signal can be extremely broadband (plus: have to support legacy systems)
 - Spec: max(BLW) vs. transmission rate
 - Test: use OIF short-stress patterns

• BLW "compensation"

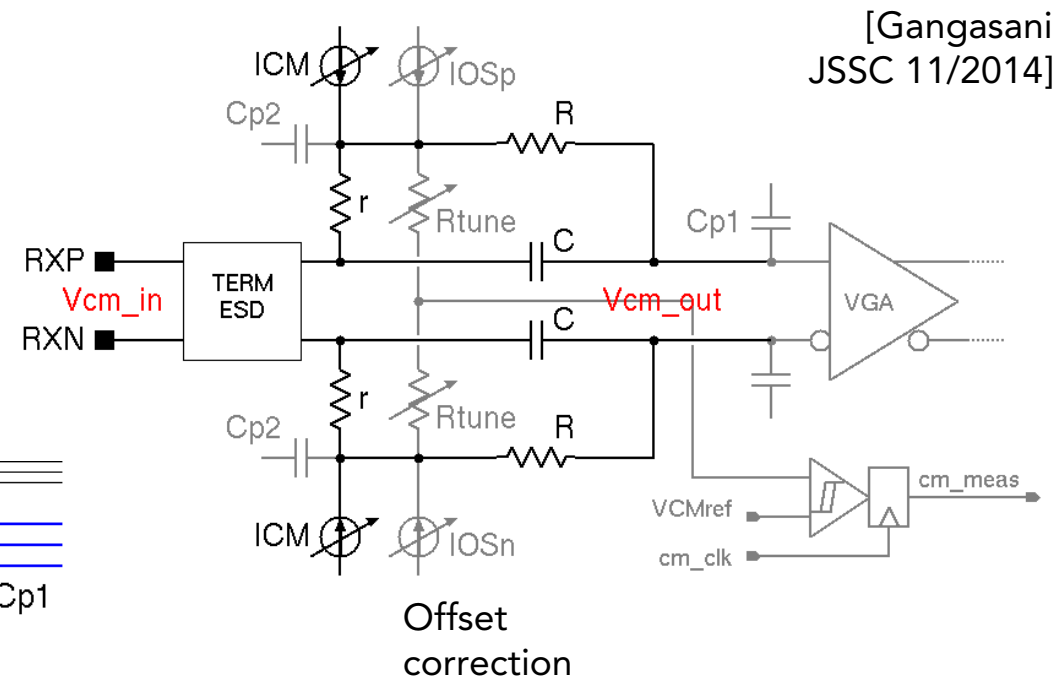  - Can compensate BLW or avoid it altogether (IBM solution)
- Level-shift signal directly from the pads (in a controlled loop)
- Avoid discharge path by using floating voltage generators




RX → AFE → Variable Gain Amplifier (VGA)

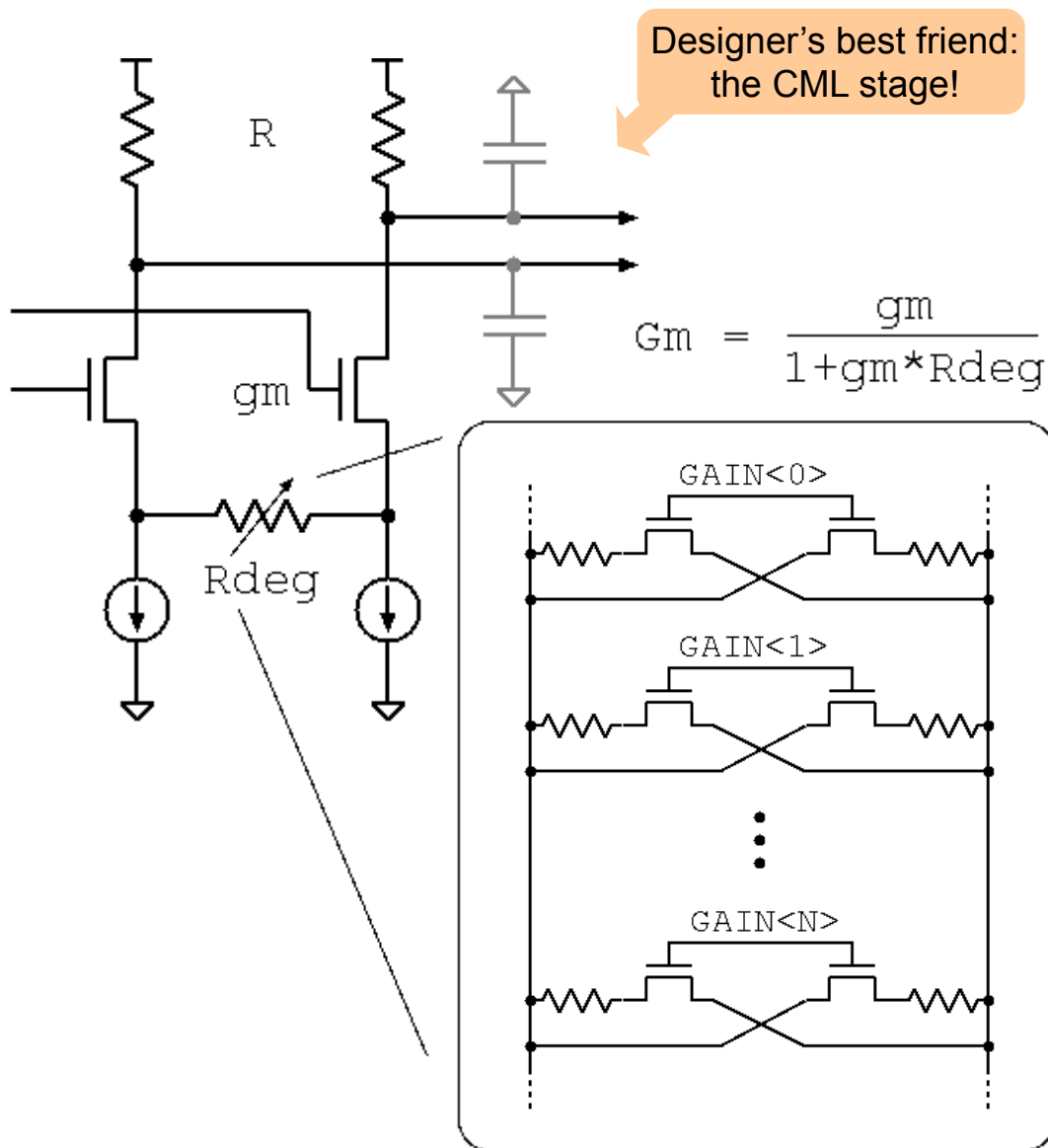


- Function: Variable gain
 - Supports AGC
 - Typical range: 10dB (in steps of 1dB)
 - Difficult to do more due to: UWP, source impedance
 - Typical gain: as much as you can get
 - Difficult to do more than ~6dB (with single CML stage across PVT corners)
- Band broadening techniques
 - Shunt/series peaking, T-coils, etc.
 - Active inductors
 - Anti-miller caps
 - Degeneration by-pass (not for VGA!)
 - Negative caps
 - ...be careful with ringing behaviour!
- Unwanted Peaking (UWP)
 - Unavoidable as much as parasitic cap!
 - Problem if system assumes orthogonal controls for gain/peaking
 - May try to reduce it...

RX → AFE → Variable Gain Amplifier (VGA)

 


- Function: Variable gain
 - Supports AGC
 - Typical range: 10dB (in steps of 1dB)
 - Difficult to do more due to UWP, source impedance
 - Typical gain: as much as you can get
 - Difficult to do more than ~6dB (with single CML stage across PVT corners)
- Band broadening techniques
 - Shunt/series peaking, T-coils, etc.
 - Active inductors
 - Anti-miller caps
 - Degeneration by-pass (not for VGA!)
 - Negative caps
 - ...be careful with ringing behaviour!
- Unwanted Peaking (UWP)
 - Unavoidable as much as parasitic cap!
 - Problem if system assumes orthogonal controls for gain/peaking
 - May try to reduce it...

RX → AFE → Variable Gain Amplifier (VGA)

 









- Function: Variable gain
 - Supports AGC
 - Typical range: 10dB (in steps of 1dB)
 - Difficult to do more due to UWP, source impedance
 - Typical gain: as much as you can get
 - Difficult to do more than ~6dB (with single CML stage across PVT corners)
- Band broadening techniques
 - Shunt/series peaking, T-coils, etc.
 - Active inductors
 - Anti-miller caps
 - Degeneration by-pass (not for VGA!)
 - Negative caps
 - ...be careful with ringing behaviour!
- Unwanted Peaking (UWP)
 - Unavoidable as much as parasitic cap!
 - Problem if system assumes orthogonal controls for gain/peaking
 - May try to reduce it...

 RX → Cont. Time Linear Equalizer (CTLE/LTE)



- Passive/Active
- Voltage/Current mode
- Active feedback
- Split path



RX → Cont. Time Linear Equalizer (CTLE/LTE)

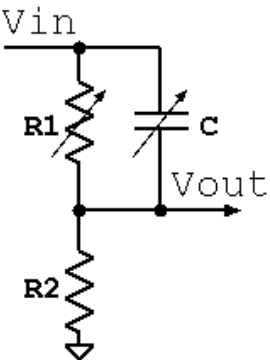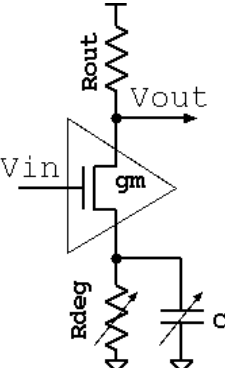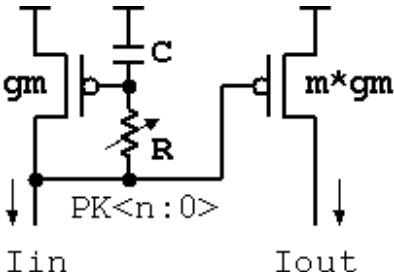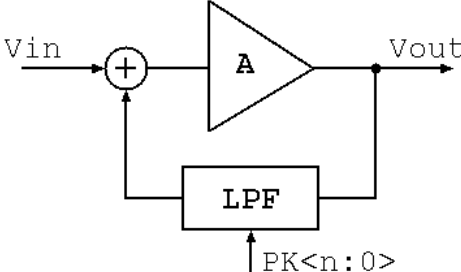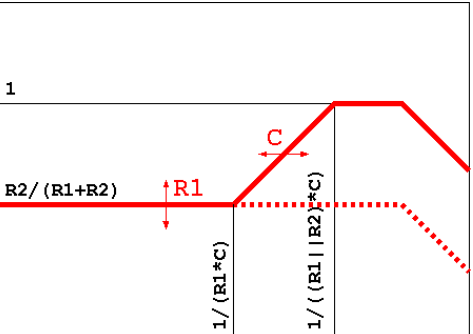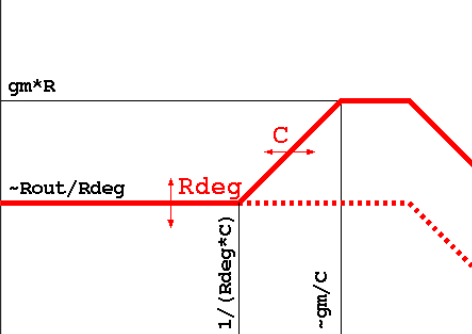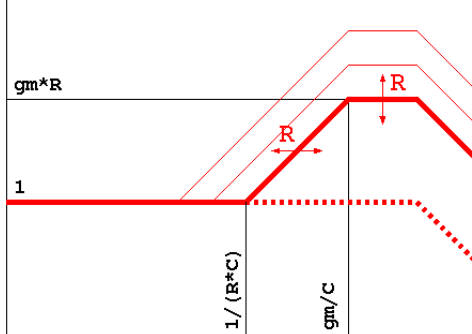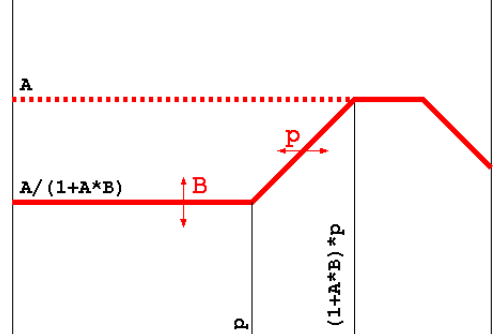	Active		
Passive	Gm-degeneration	Current-mode	Active-feedback
			
			

Most important requirements:

- High-frequency boost
- Minimal low-frequency loss
- Good linearity
- Well-behaved phase response (limited usage of resonant peaking)
- Tunability of the boost
- Low input capacitance (ultimately determining S11)

 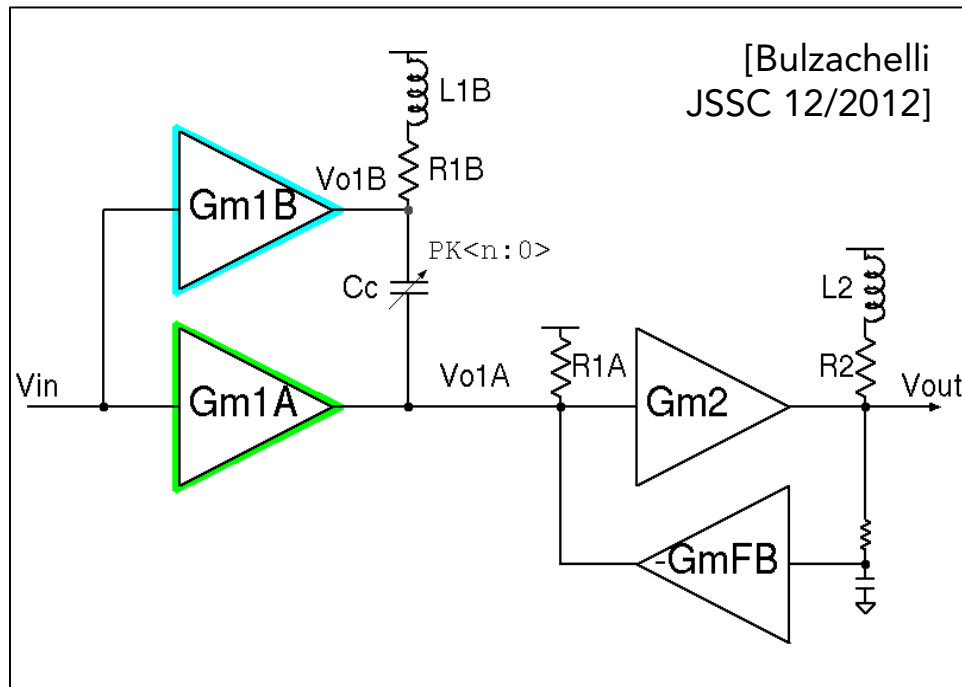RX → Cont. Time Linear Equalizer (CTLE/LTE)





- Peaking amplifier (= active, linear)
 - Split path + AC-coupling
 - Inductive peaking
 - Active feedback



$$\frac{V_{o2}}{V_{in}} = \left(\frac{GA \cdot G2}{1 + GFB \cdot G2} \right) \cdot \frac{1 + s \cdot Cc \cdot R1B \cdot \left(1 + \frac{Gm1B}{Gm1A} \right)}{1 + s \cdot Cc \cdot R1B \cdot \left(1 + \frac{R1A/R1B}{1 + GFB \cdot G2} \right)}$$

$$\delta P = \frac{P_{max}}{P_{min}} = \frac{G_{\infty}(Cc = max)}{G_{\infty}(Cc = 0)} = \frac{\left(1 + \frac{Gm1B}{Gm1A} \right)}{\left(1 + \frac{R1A/R1B}{1 + GFB \cdot G2} \right)}$$

 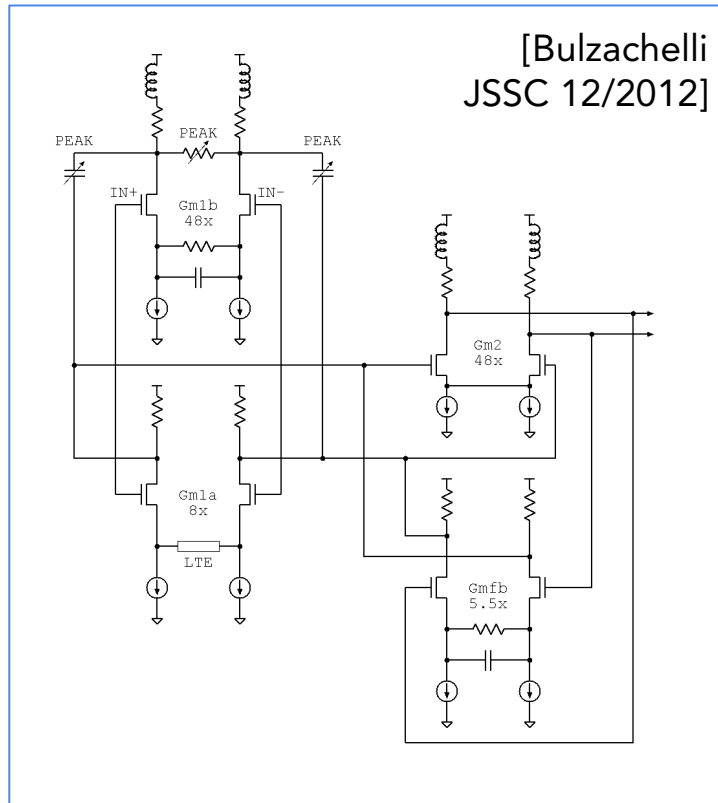RX → Cont. Time Linear Equalizer (CTLE/LTE)



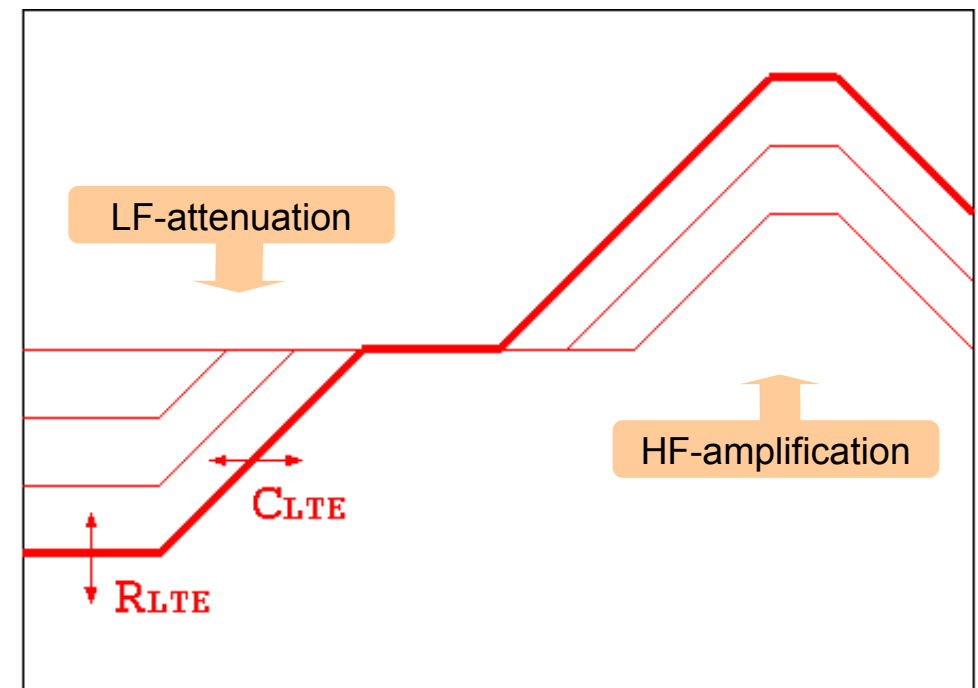
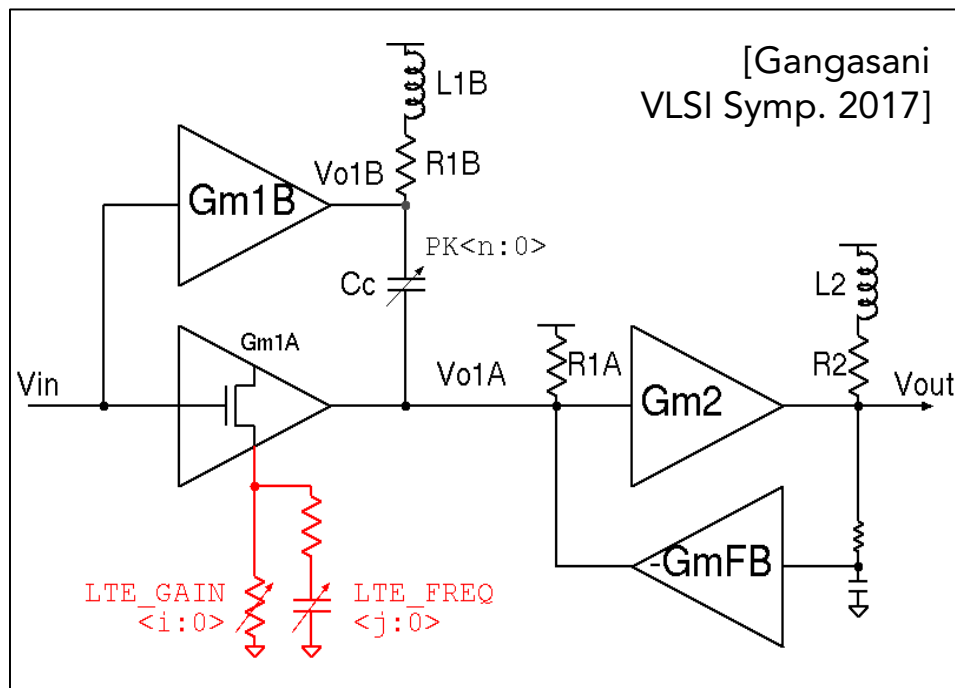
RX → Cont. Time Linear Equalizer (CTLE/LTE)




- LTE effectively **increases the equalization capability** by combining LF-dump & HF-boost (plus: **approximate slopes different than 20dB/decade**)
- CTLE/LTE: low-frequency shaping and large BW → **often require bulky passive devices (RLC)**, tends to become a luxury in modern technologies optimized for digital

RX → Cont. Time Linear Equalizer (CTLE/LTE)


[Gangasani
VLSI Symp. 2017]

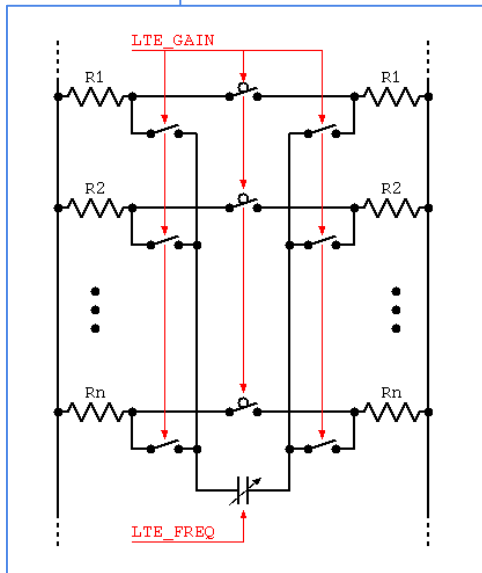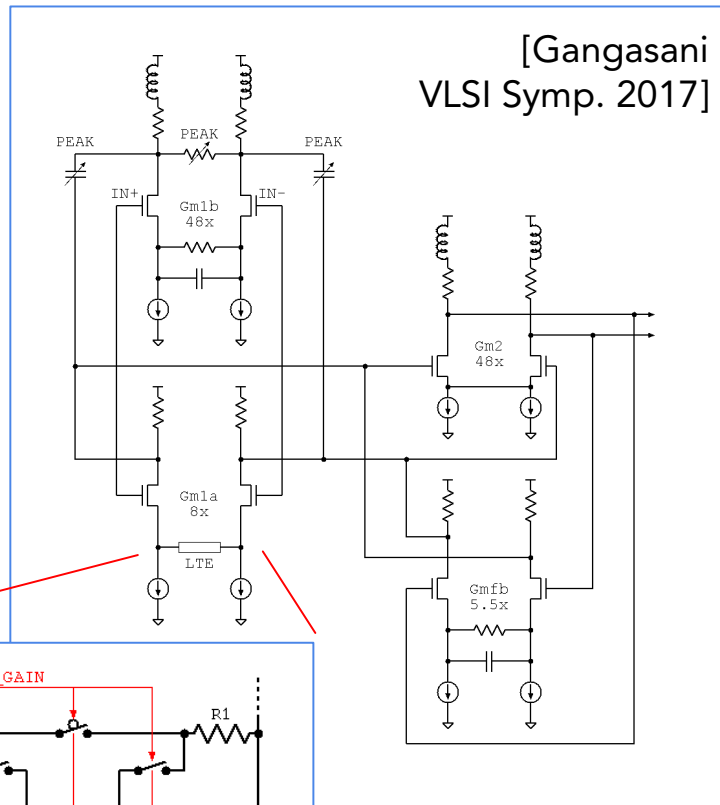

AC-RESPONSE

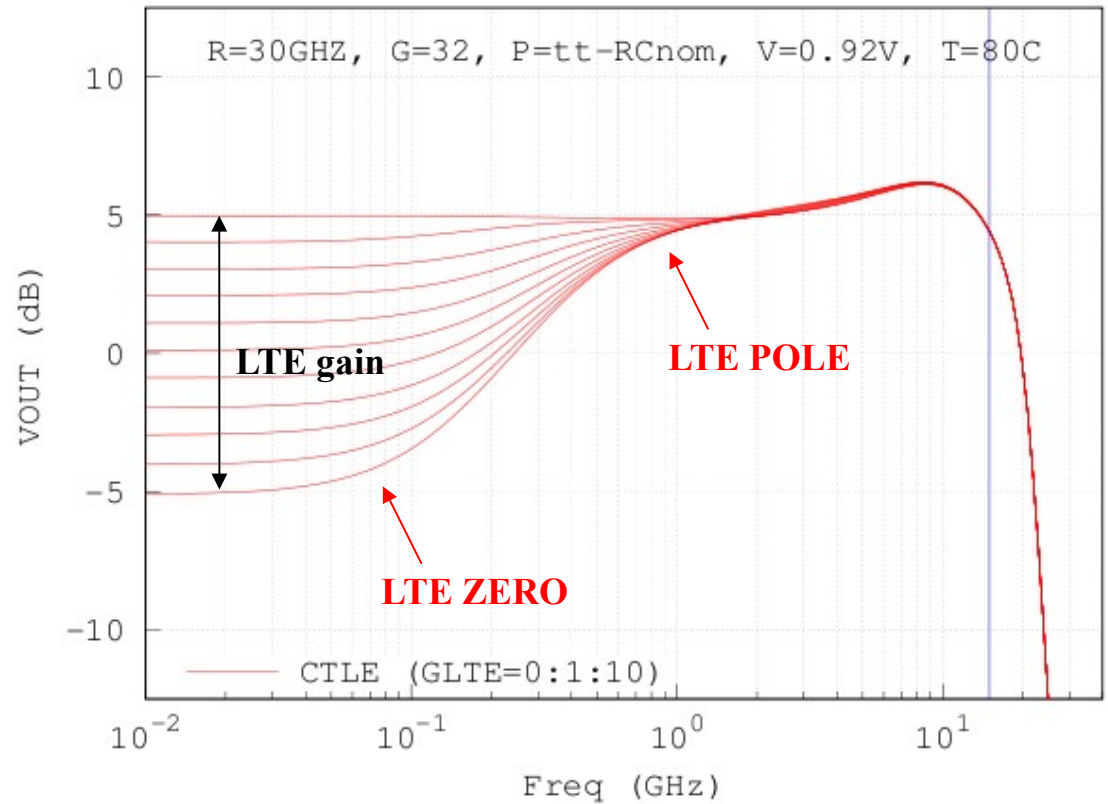


RX → Decision Feedback Equalizer (DFE)

 

- Speculation
- Sub-rates
- Summer
- Slicer

RX → Decision Feedback Equalizer (DFE)

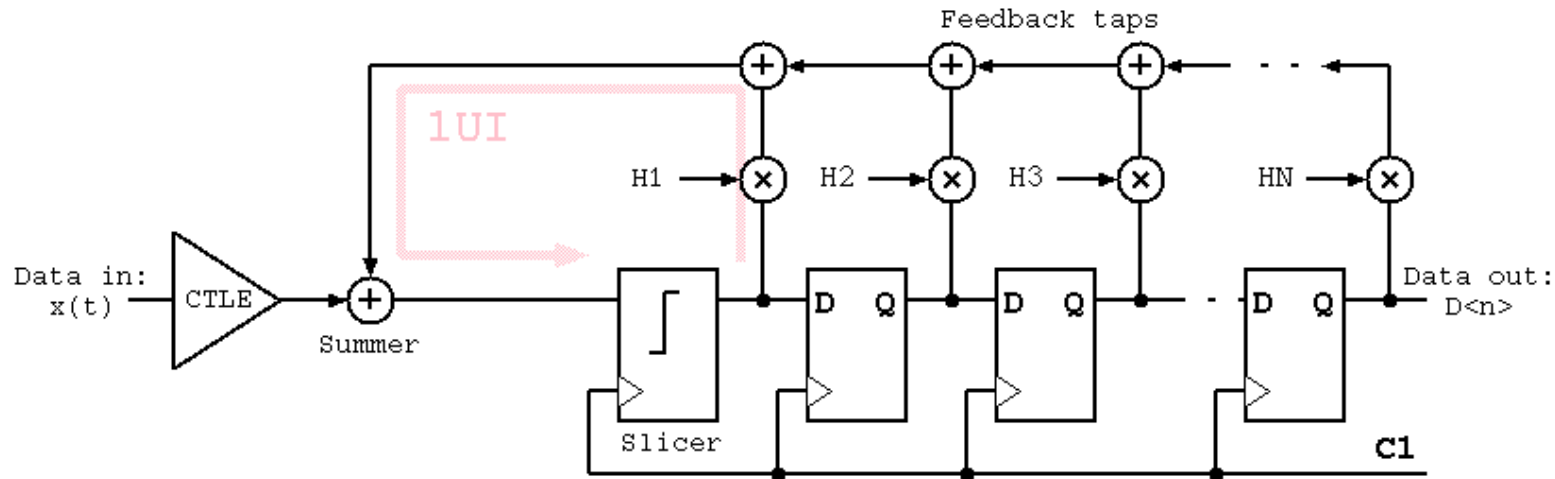


- DFE is powerful but difficult at those speeds! (it's a **feedback loop**)
 - 1-UI for decision, feedback and summation: 31.25ps if running @ 32Gbps
 - Typical slicer decision time for 10mV amplitude is ~30ps (in 14nm CMOS)
 - Typical inverter delay is ~9ps (in 14nm CMOS)
 - Summation settling time with 15GHz BW is ~22ps

However you turn it, this ends up being much longer than 1 UI !

RX → DFE → Unrolling

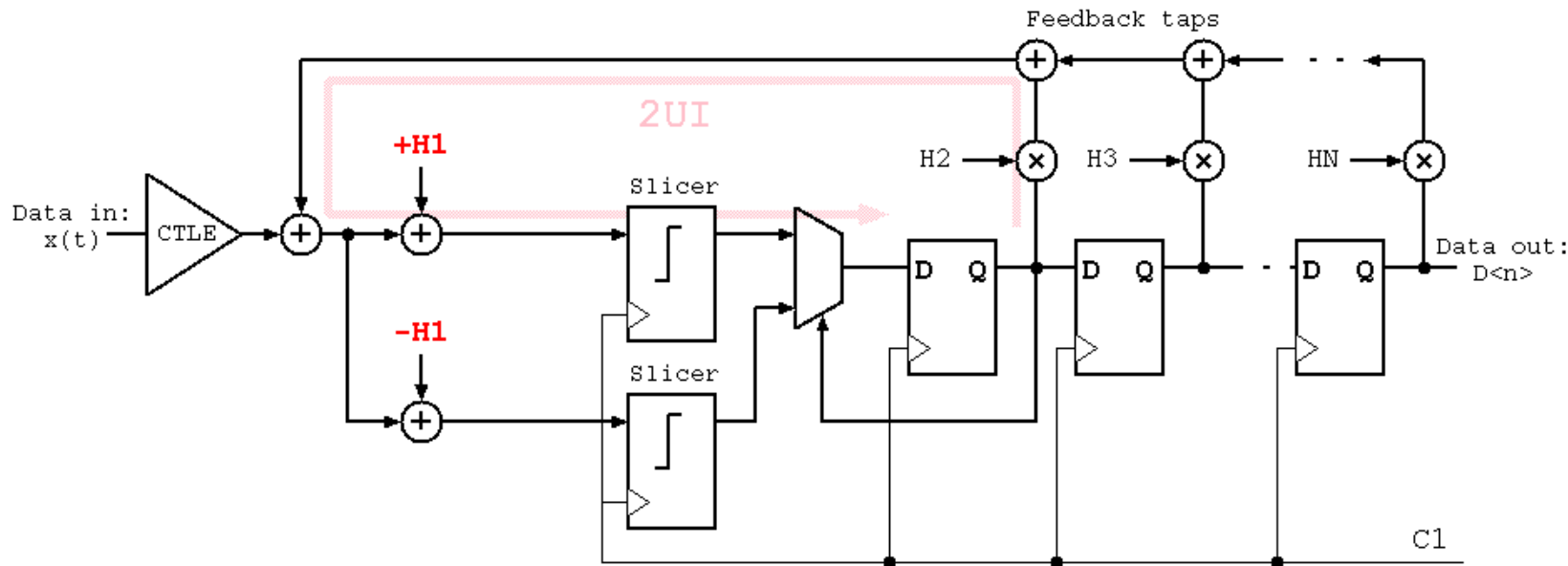
- We could borrow 1 bit time:
 - Take both decisions and choose when the next bit comes
 - This is **1-level look-ahead** (also called “speculation” or “unrolling”)
 - Buys us 1 UI time at the cost of added hardware
 - Sounds fishy? It does work!



- You can take it further: 2-levels (4 decisions), 3-levels (8-decisions), ...
- But: at each unrolling step you are doubling the number of slicers (4x for PAM4)
 - Additional load for the driving stage and for clock distribution
 - Are you also doubling the number of summers? Prefer to shift the slicing thresholds

RX → DFE → Sub-rate clocks

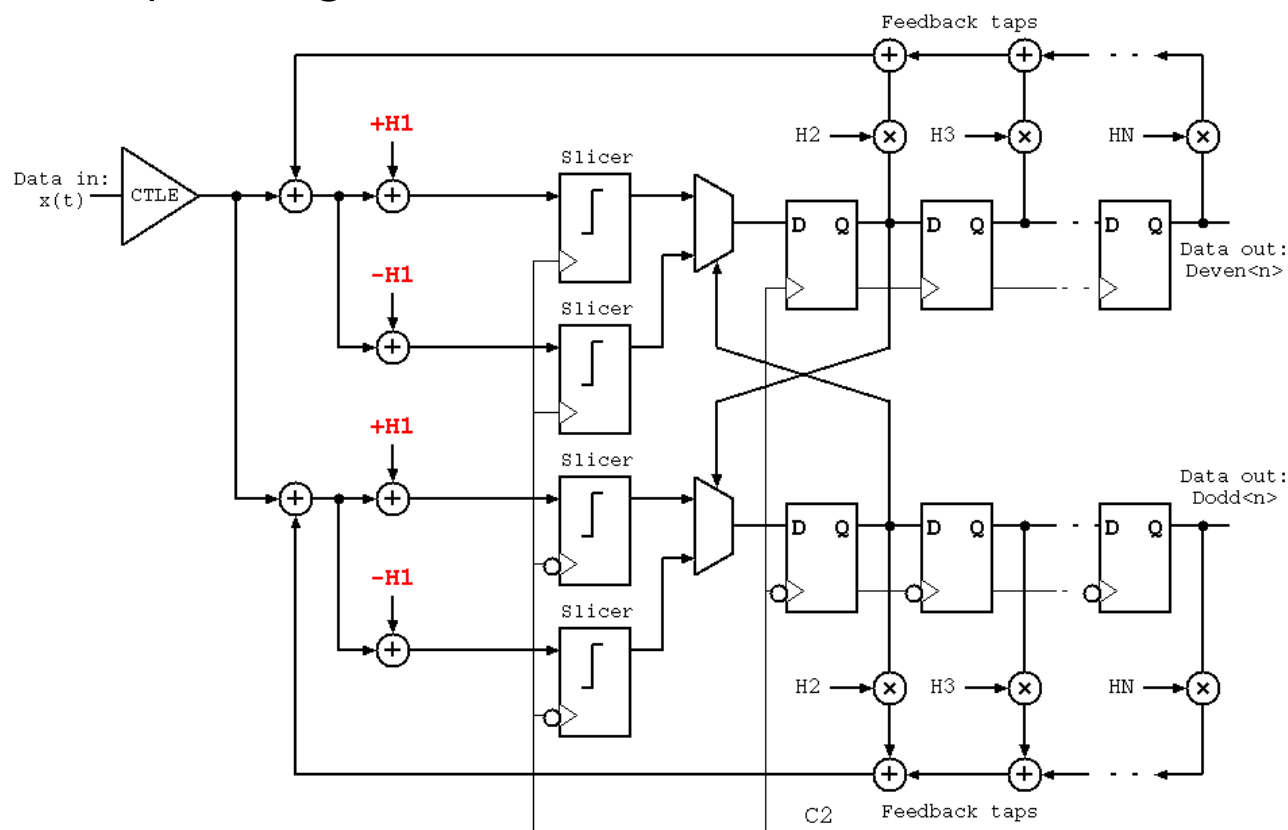
- Half-rate (C2)
 - Further relax the circuit requirements by halving the clock frequency and processing the data on 2 parallel paths (phase shifted by 180°)
 - Need to insure duty-cycle accuracy of the C2 clocks
 - Where does the power go? ...




- Quarter-rate (C4)
 - Need to insure quadrature accuracy of C4 clocks, etc.

RX → DFE → Example

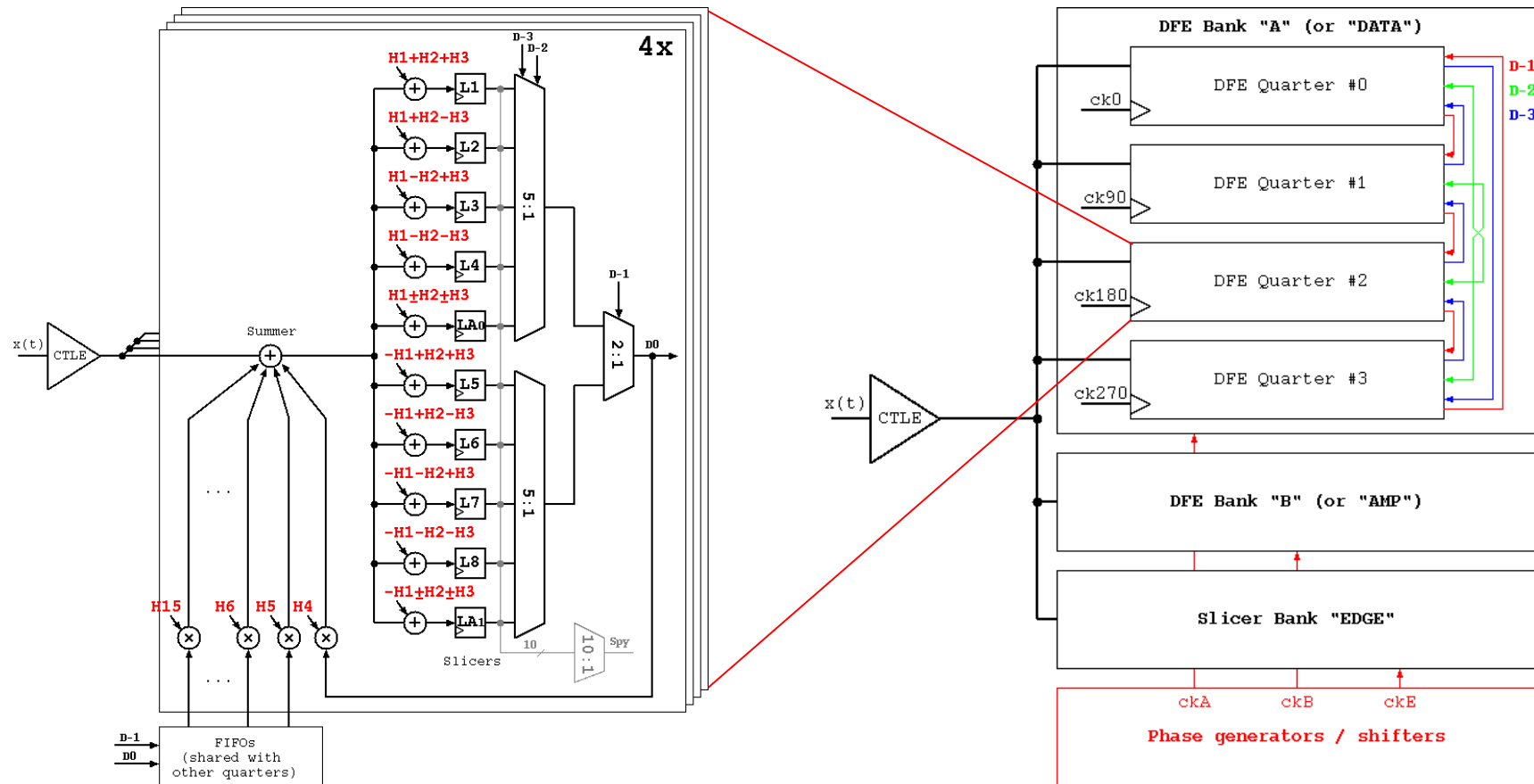- Quarter-rate triple-speculation 15-taps DFE for 32Gbps NRZ



 - Must provide measurement channels
 - Latch calibration (offset)
 - DFE taps adaptation
 - Phase detection
 - Test & monitoring




- Redundant banks and/or latches
 - A/B/EDGE
 - DATA/AMP/EDGE
 - Redundant latches (spy) that can be cycled

[Bulzacchelli VLSI Symp. 2017]

RX → DFE → Summer


- Resistively loaded CML summer

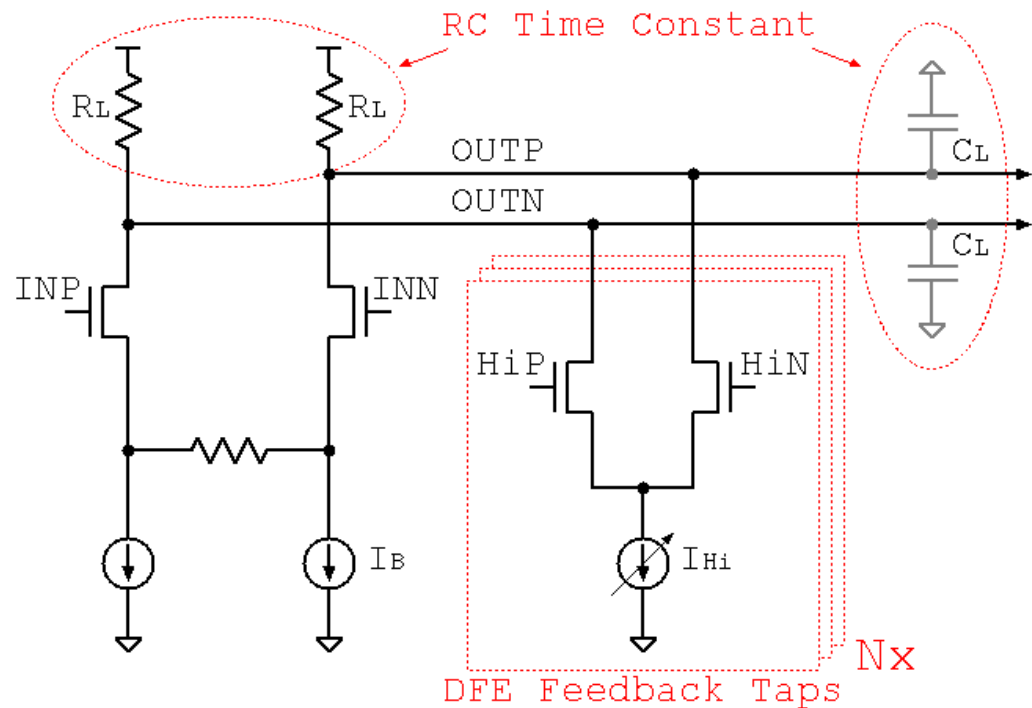


- Current summation implements: signal (linear) + feedback taps
- Tap amplitudes are tuned with the tail currents (I_{Hi}) through IDACs
- Required timing sets a limit to max. R_L and min. I_B (\Rightarrow min. power)

RX → DFE → Summer

- Current integrating summer

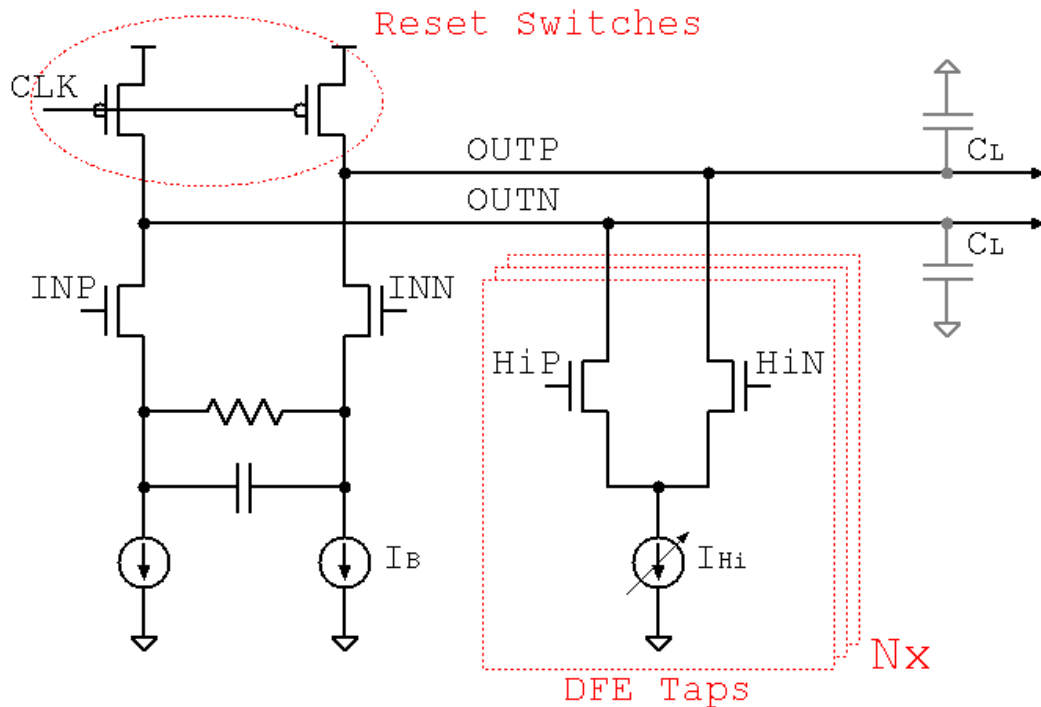


[Park ISSCC 2007]

 

- By replacing resistors with PMOS switches, the I_B current can be scaled
- Highest efficiency if only parasitic CL is loading the output, however also highest variability => requires calibration
- Feedback taps (HiP/N) should be established before beginning of integration
- Peaked integrator vs. Sampled integrator? (see next slide)

RX → DFE → Summer

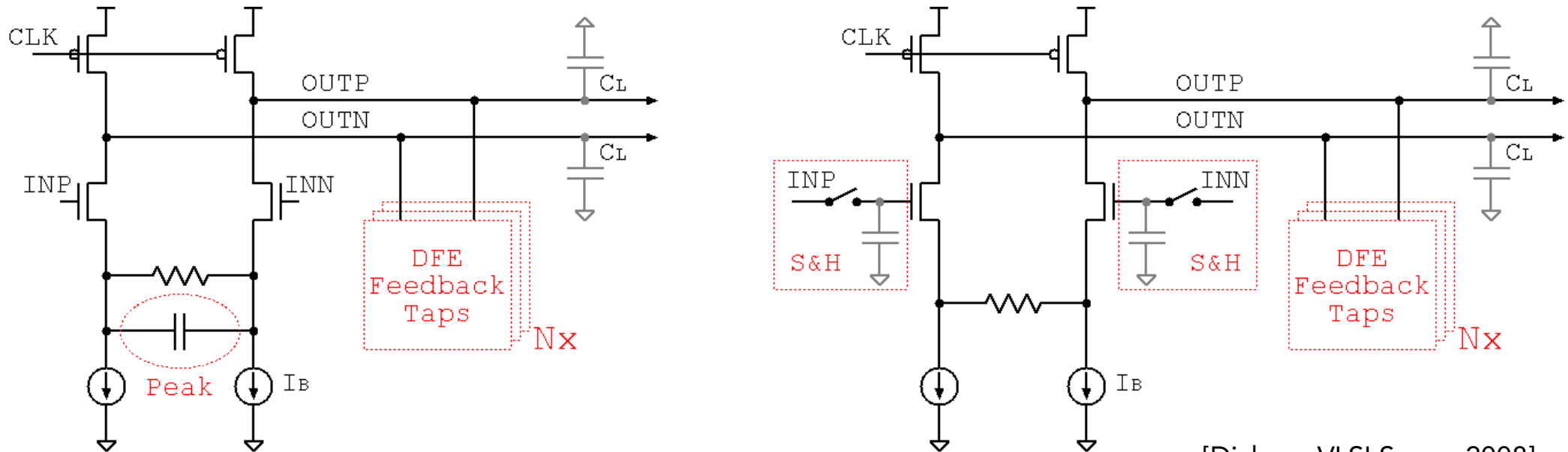- Peaked integrator vs. Sampled integrator?





[Dickson VLSI Symp. 2008]

- The integration is an average over the clock cycle ("sinc" loss vs. frequency)
 - Zero transmission (infinite loss) at clock frequency (F_{baud}), 3.9dB loss at $F_{\text{baud}}/2$, etc.
- Peaked integrator
 - Compensates sinc loss with capacitive peaking
 - Integration time is $1UI$ (cannot increase gain by increasing integration time)
- Sampled integrator
 - Integrates a sampled (=constant) version of the signal
 - Problems related to sampling noise (kT/C), kick-back, ...
 - May allow longer integration times (with lower current) in sub-rate systems (e.g. C4)

RX → DFE → Summer

 
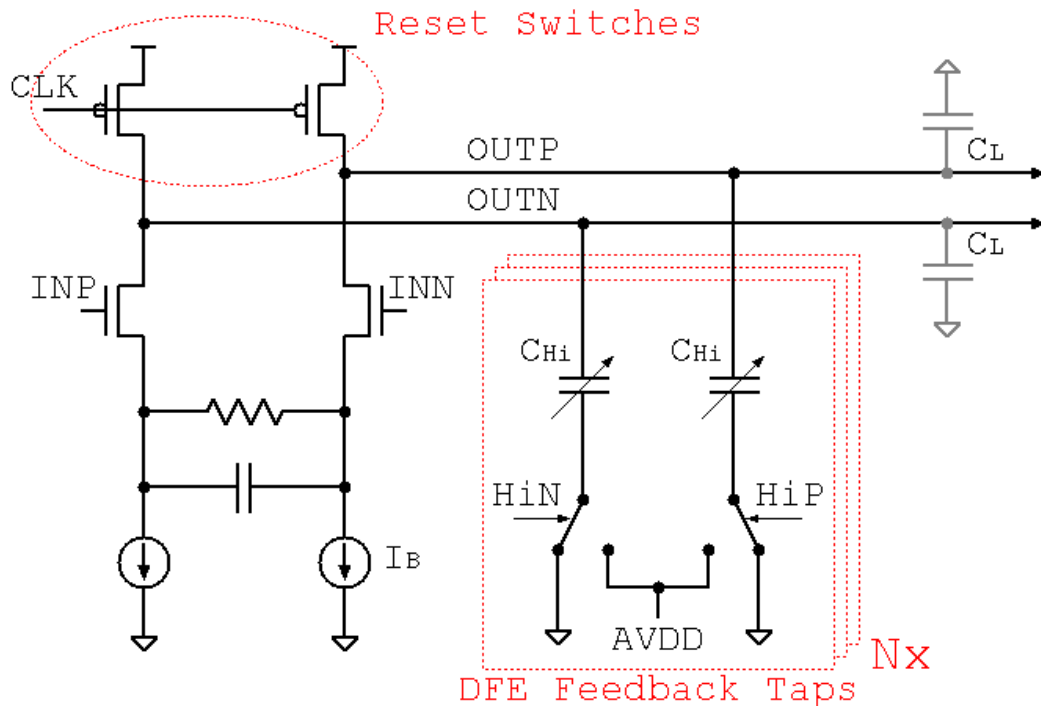
- Integrating summer with capacitive charge feedback



[Toifl VLSI Symp. 2011]

- Charge injection allows to relax the timing
- Feedback tap need not be ready before integration starts
- Tap amplitudes are tuned with the feedback caps (CHi) through CDACs
- Depending on technology: may end up being bulky/parasitic
 - Usually reserve it for the first non-speculated tap (most timing critical)

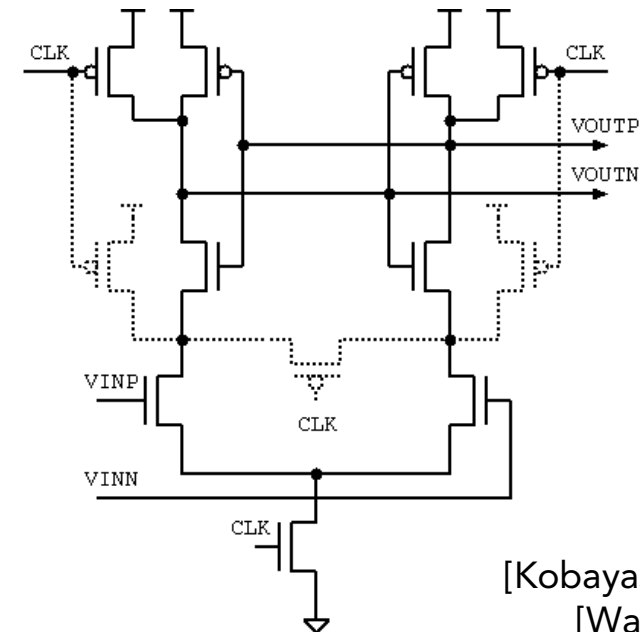 - Threshold detection (sensing) & Sampling
 - In practice these 2 functions are merged in the clocked-comparator (or "latch")




[Kobayashi JSSC 1993]
[Wang JSSC 2000]

- CML latch
 - Trade-off between power and speed
 - Draws static current
 - Reduced swing output levels

- StrongARM latch (=DCVS)
 - Power efficient due to regenerative amplification
 - No static current
 - CMOS output levels
 - Intrinsically faster

Adaptive Equalization




- Why adaptive?
 - In most applications the channel characteristic is not known a-priori
 - Marketing requires covering a large spectrum of applications anyway (same IC)
 - Slowly varying channel characteristic (temperature, humidity, aging, etc.)
- Different approaches
 - Least Mean Square (LMS) and Recursive Least Square (RLS) algorithms
 - Spectrum balancing (CTLE/LTE)
 - DFE taps = negative post-cursors in the pulse response (if possible to measure)
 - Zero-forcing on crossings (maximize eye width)
 - Zero-forcing on data (maximize eye height)
- TX-FFE
 - If EQ is done in the TX, it is difficult/costly to “close-the-loop” for adaptation
 - Mostly open-loop (operator driven) configuration

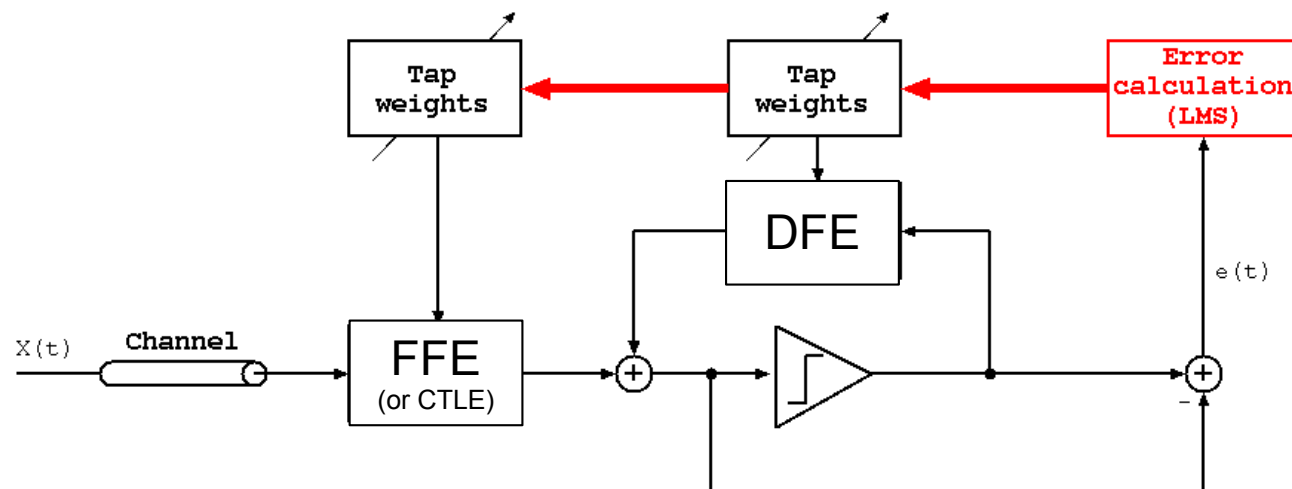

Other system impairments

BER strongly depends on SNR:
 $BER = \frac{1}{2} * \text{erfc}(\text{SNR}/2)$

- Sources of errors (reducing SNR, one way or the other)
 - Reflections & Crosstalk
 - Attenuation (insertion loss)
 - Amplitude noise, linear distortion & offset (before slicer)
 - Sampling clock jitter (phase noise) -> reduces SNR, due to non-optimum sampling point
 - Process/Environment variation (PVTs) and device aging
- Avoid/Correct wherever possible
 - Broadband TX/RX termination (for low reflections)
 - Signal conditioning (enhance signal wrt. comparator sensitivity/noise)
 - Offset correction
 - Clock duty-cycle correction (for half-rate and lower)
 - Clock quadrature correction (for quarter-rate and lower)
 - startup / background calibration

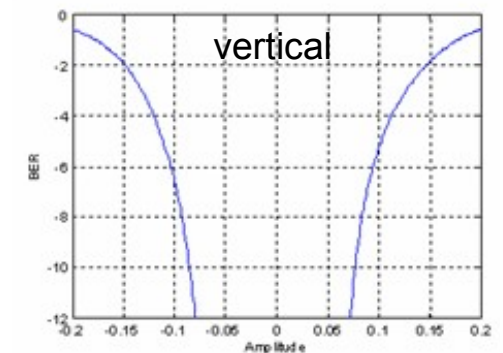 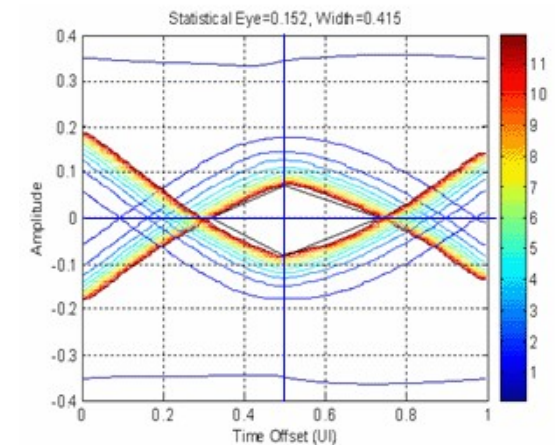


SERDES design in advanced CMOS



- Motivation & Challenges
- Architectural solutions
- Implementation details
- **Future trends & remarks**



Market pushing for 56-112-224Gbps!

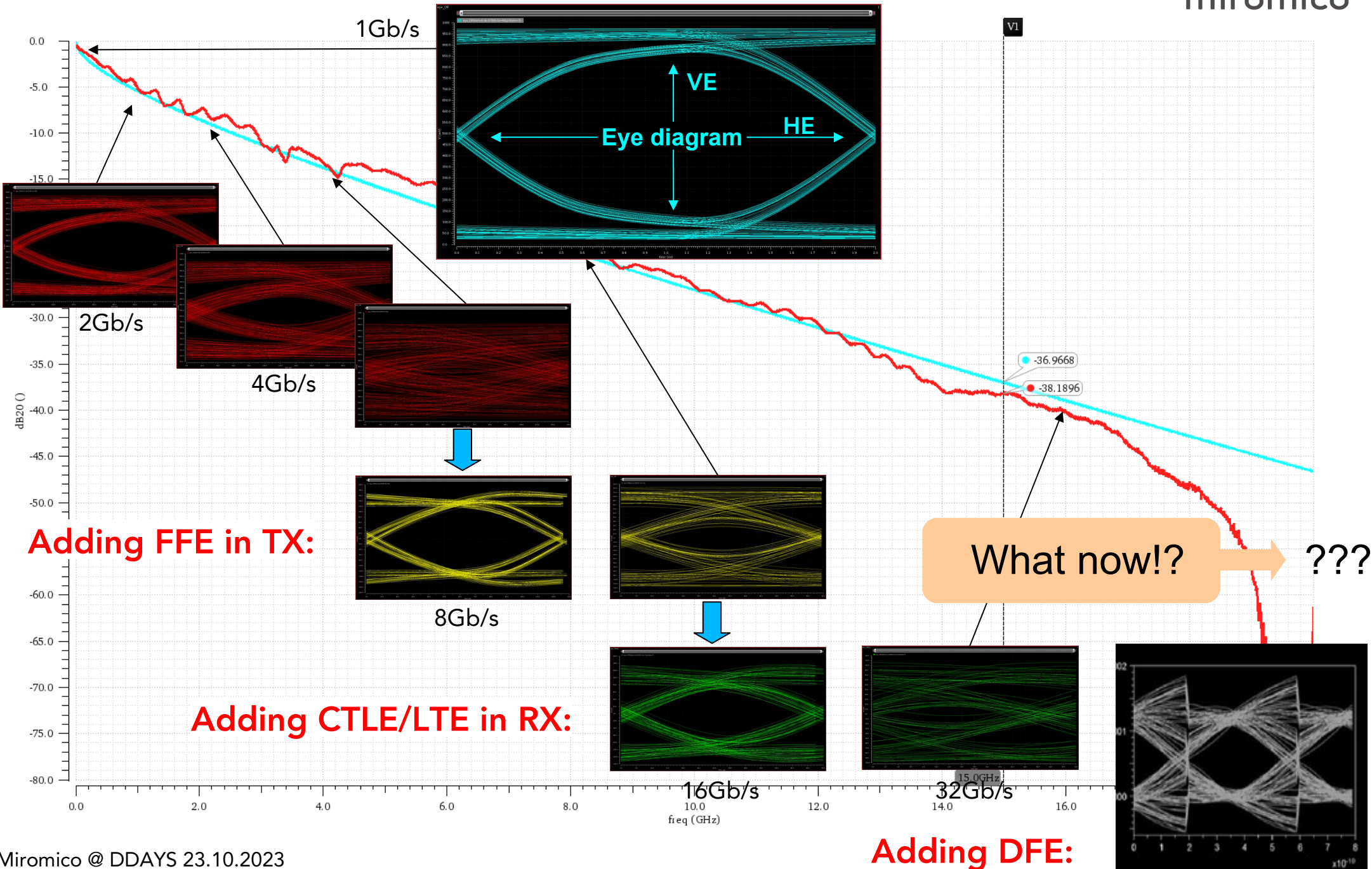

Alternative modulation schemes

Instead of going faster, send more information at the same baud-rate!

- NRZ (aka. PAM-2)
 - Binary levels
 - One transition per bit (higher BW requirements wrt. multi-level schemes)
 - Profits of the full voltage amplitude
- PAM-4
 - Quaternary levels
 - Requires half of the bandwidth (wrt. NRZ) for the same bit rate
 - ~9.5dB SNR penalty due to more levels in the same voltage amplitude
 - More complex implementation (esp. for Sampling, EQ, CDR, ...)
- NRZ vs PAM-4?
 - Forced choice, in case you must comply with a given standard
 - Depends (mainly, but not only) on the channel
 - Compare the channel loss at double the frequency vs. the 9.5dB SNR penalty coming from PAM4 (usually consider ~11dB or higher to account for higher complexity, sensitivity, etc.)
 - Implementation preferences...

 
 


PAM-4 is usually accompanied by improved error-correction coding

- Forward Error Correction compensates for higher sensitivity of PAM-4
 - FEC codes allow to dramatically reduce required BER (for same channel loss) or allowed channel loss (for same BER). Recover from $10e-5$ BER to $10e-15$
 - Expensive: large amount of logic, additional latency (though becoming better with new technologies, new schemes, etc.)
- Other encoding schemes also used for
 - Improving DC balance
 - Ensuring minimum transition rate for clock recovery
- Overhead (redundant bits) and code "efficiency"
- Some popular schemes
 - 8/10b, 64/66b, Reed-Solomon(n,m), ...



DAC/ADC based transceivers

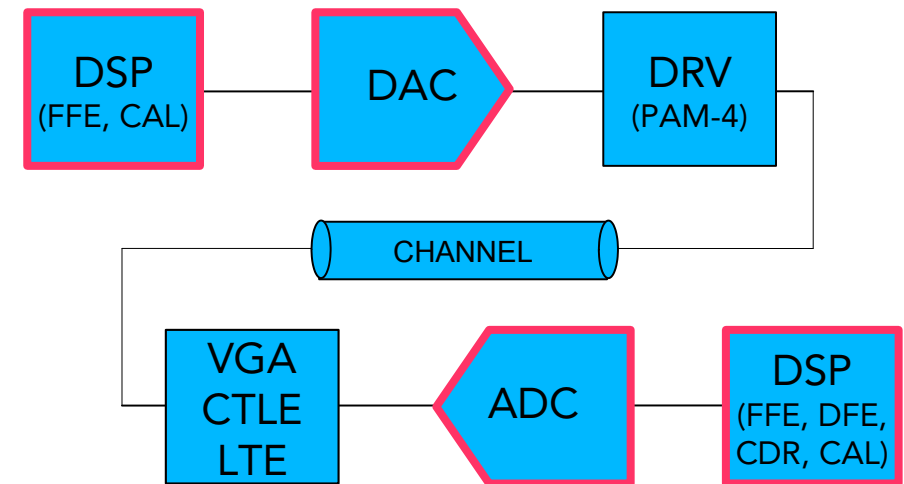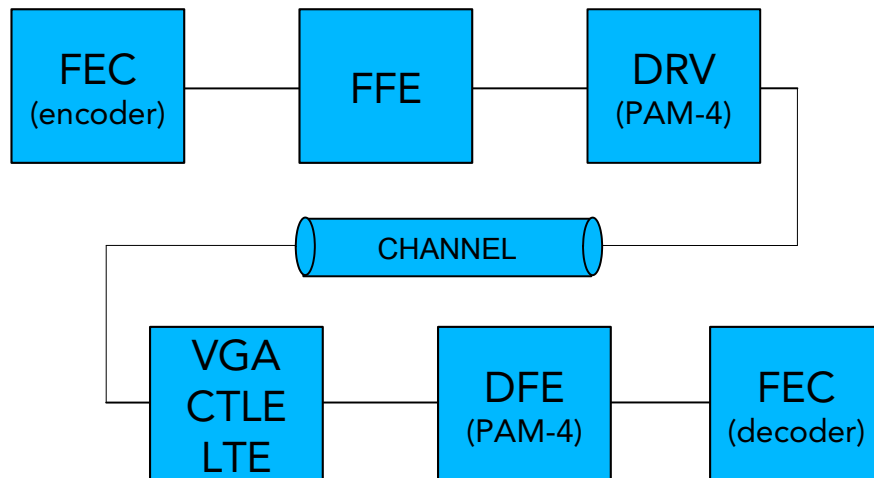

- Slicer-based RX

- Mature architecture, can be made very efficient
- DFE-loop timing can drive power very high as the transmission rates keep increasing
- Complexity and power explode with multi-level modulation (PAM-4)
- Does not scale well in technologies where Ft & RC bandwidth don't scale correspondingly

- ADC-based RX (& DAC-based TX)




- Push EQ on the digital side (scalable, portable, versatile, etc.)
- Intrinsically compatible with multi-level signaling (PAM-4/8/...)
- Enables more complex EQ in DSP
- Analog EQ still beneficial to reduce requirements on ADC resolution
- Analog calibration enables "digital-like" scaling of DAC/ADC front-ends
- Better power trade-off for modern technologies, higher data-rates, more stringent EQ requirements

Generalized differential signaling

- Research effort to improve bitrate/pin efficiency wrt. differential pairs
 - Single-ended: 1 bit every clock cycle over 1 wire (ratio: 1) → **Most efficient, BUT not differential!**
 - Differential pair: 1 bit every clock cycle over 2 wires (ratio: 0.5)
 - MIPI C-PHY: 2.28 bits every clock cycle over 3 wires (ratio: 0.76)
 - Kandou Chord Signaling (eg. ENRZ, EP3L, CNRZ, ...)
 - ENRZ (= Ensemble-NRZ): 3 bits every clock cycle over 4 wires (ratio: 0.75)

Wire State	Receiver Output		
	A-B	B-C	C-A
+x	1	0	0
-x	0	1	1
+y	0	1	0
-y	1	0	1
+z	0	0	1
-z	1	1	0

MIPI C-PHY

  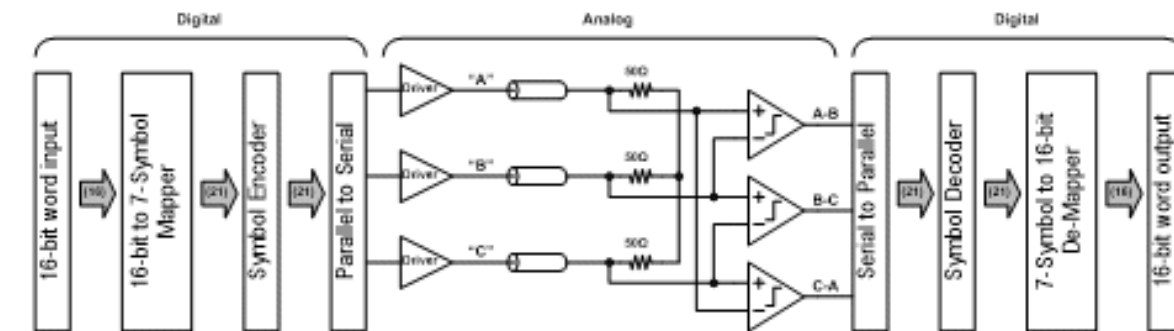

[<https://www.design-reuse.com/articles/43501/mipi-d-phy-c-phy-combo-type-architecture.html>]

Do you see the light?

- Optical is slowly but steadily replacing copper for long-reach interconnects:
 - Legacy support is keeping us electrical as long as possible
 - Huge investments have been made in existing infrastructures
 - Electrical-to-optical interface is still somehow exotic
 - Integration of modulators, filters and photo-diodes requires large areas
 - Mechanical mounting of the couplers clashes with the heat-sinks or the PCB
 - Difficult to reach the same integration density as the current electrical solutions
 - On-chip purely optical processing isn't a thing yet; we still rely on the good old silicon transistor to do the heavy lifting
- But certainly:
 - Long Reaches (LR) are becoming increasingly difficult on electrical conductors
 - E-O interfaces are moving closer to our chips (inside the package? inside the IC?)
 - Increasing pressure on XSR (and USR) links: chip-to-(optical)module

Transmission over existing copper cables still possible thanks to sophisticated (but inexpensive) silicon solutions, such as coding/equalization schemes and error correction algorithms of ever increasing complexity!

And of course there is more to SERDES design than just EQ...

EQ

FFE
CTLE
DFE
(others?)

TERM/ESD

Line impedance termination
ESD protection
AC-coupling

Continuous adaptation

CTLE peaking regulation
FFE/DFE coefficients

AGC

Programmable amplification
Background gain regulation



Serialization
Deserialization

Data encoding

8/10b, 64/66b, FEC, Scrambling

CDR

Clock & Data Recovery
(data must contain traces of the clock, in the form of transitions)


Logic

Link/Application layer glue logic
Error Detection/Correction

Support functions

Offset cancellation
Clock corrections (DCC, QCC)
Monitoring and measurements
Testability

Thanks for your attention!

 

miromico

<http://www.miromico.ch>